
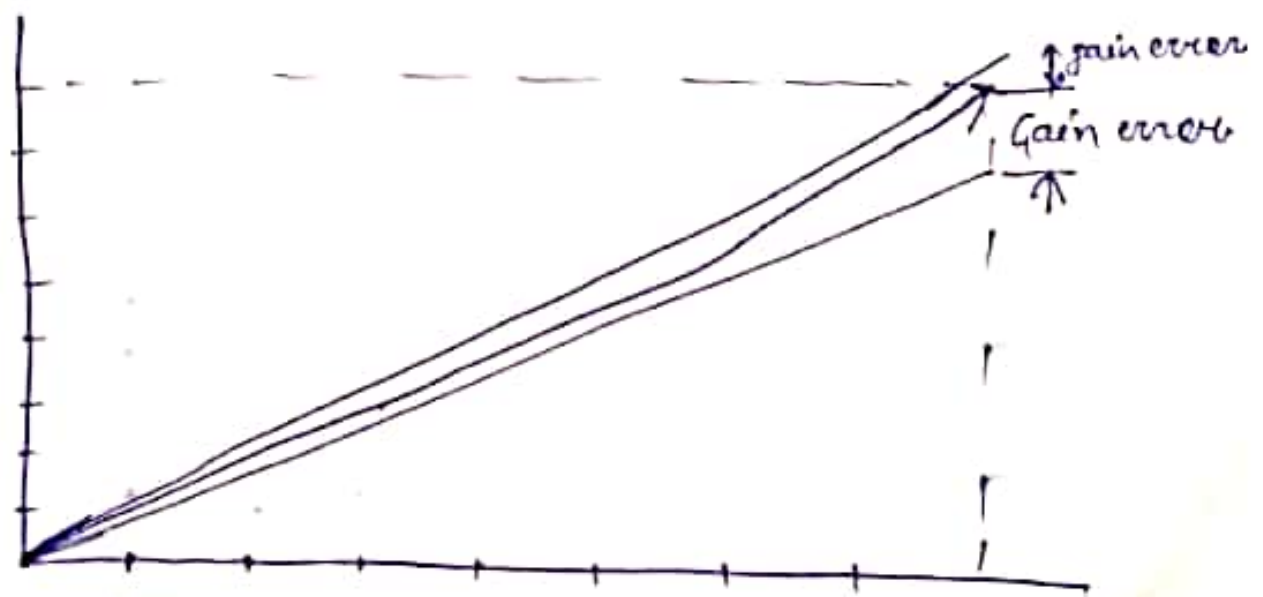
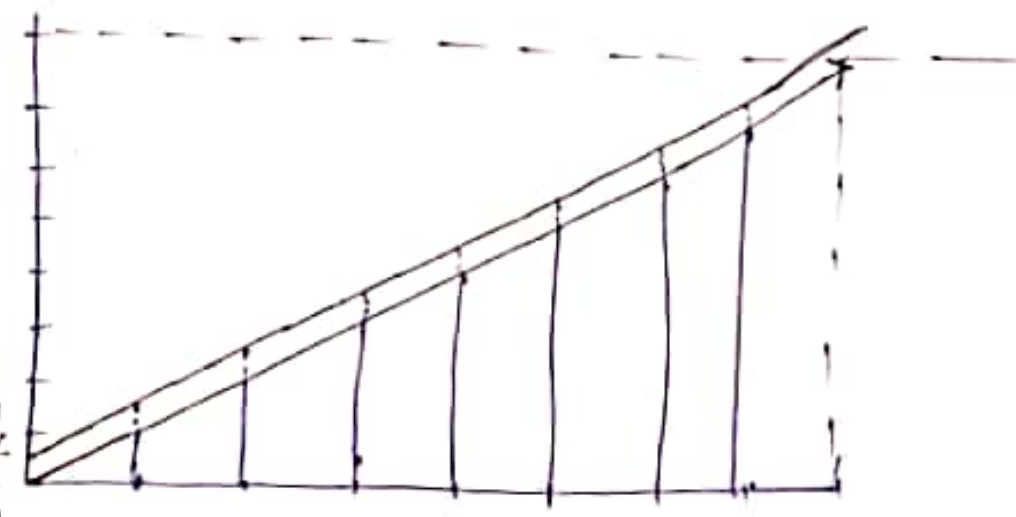


# Output-Input relationship of DAC.

## Input-output characteristics

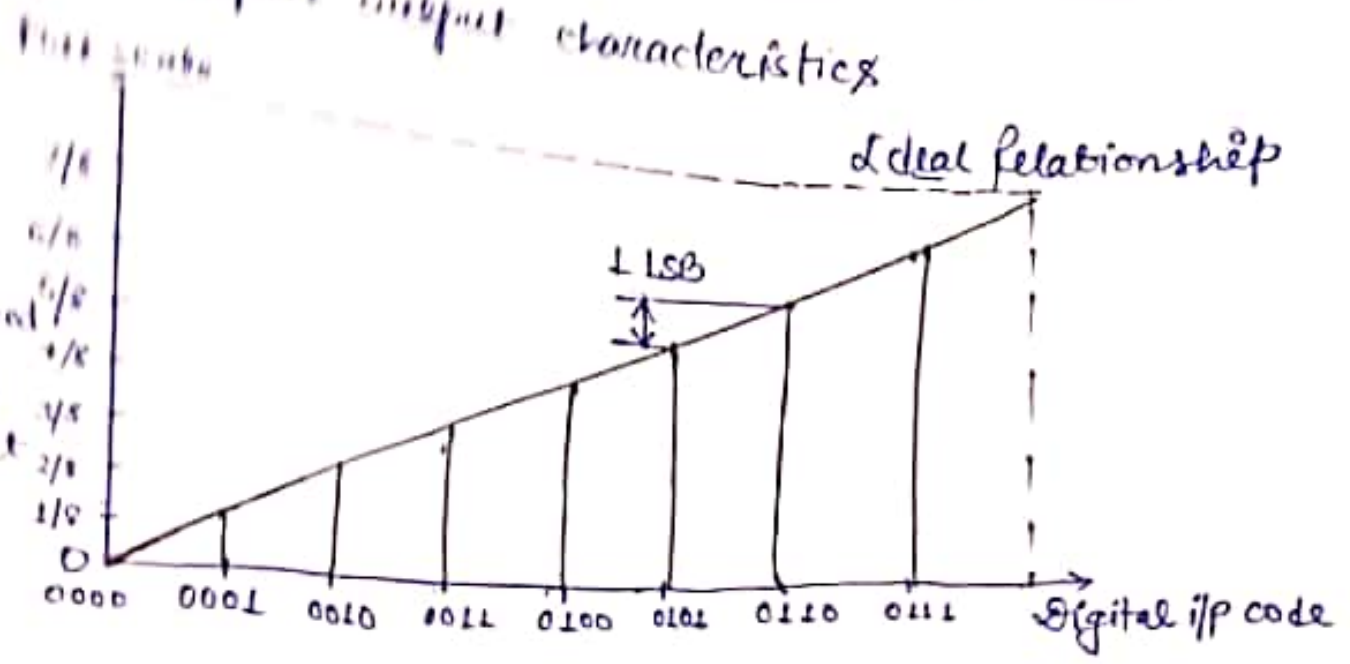

(Transfer function of DAC)

④

The output of DACs are used to drive a variety of devices.

Ex - Loudspeaker, video display, motor controller, mechanical servo, radio frequency transmitter & temperature control etc.

A DAC produces a quantized (discrete step) analog output in response to a binary digital input code.

The transfer function for an  $n$ -bit DAC is shown in previous page.

The digital input may be

TTL (Transistor-transistor logic)

ECL (Emitter coupled logic)

CMOS (Complementary Metal-oxide semiconductor)

LVDS (Low voltage differential signaling)

while analog output may be either voltage or current.

To generate the output, a reference quantity (either a voltage or a current) is divided into binary and/or linear fraction.

Then the digital input drives switches that combine an appropriate number of these fractions to produce the output.

the analog output of DAC is

$$A_0 = \frac{D_i}{2^N} R_{ref.}$$

Where  $A_0$  = Analog output

$D_i$  = Digital input code

$N$  = number of digital input bits

also,  $2^N$  = Resolution

$R_{ref}$  = Reference value (at full scale)

### Common O/A Architecture

1 Binary weighted architecture

2 voltage divider architecture

