

Name of faculty: → Er. Vijay Kr. Ram

Subject: - Analog Circuit.

(EC - 2<sup>nd</sup> yr, 4<sup>th</sup> sem.)

Query Time: → 03:00 PM - 04:00 PM.

### Amplifier Working

54

An amplifier is an electronic device that can increase the power of a signal (a time-varying voltage or current). It is a two-port electronic circuit that uses electronic power from a power supply to increase the amplitude of a signal applied to its input terminals, producing a proportionally greater amplitude signal at its output.

The amount of amplification provided by an amplifier is measured by its gain: the ratio of output voltage, current, or power to input. An amplifier is a circuit that has a power gain greater than one.

#### Classification of Power Amplifier.

— x ————— x ————— x —————



Based on conduction angle and efficiency of power amplifier.

1. CLASS A
2. CLASS B
3. CLASS AB
4. CLASS C

↓

⇒ CLASS A amplifier:

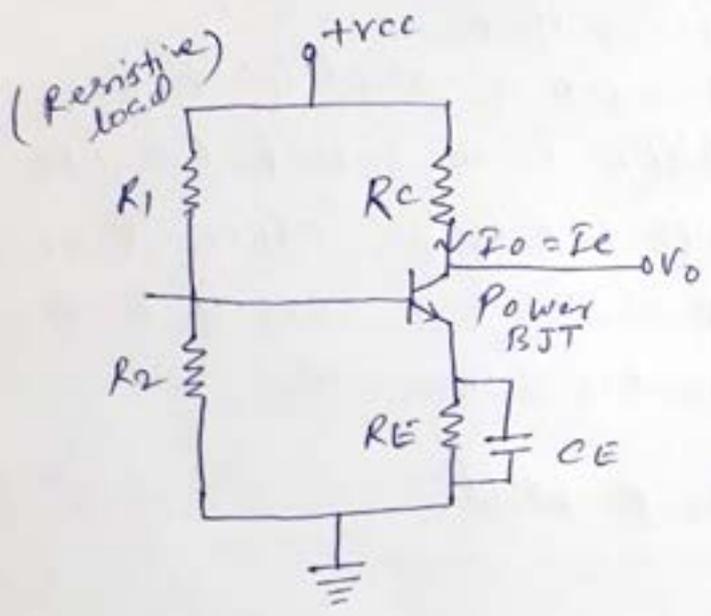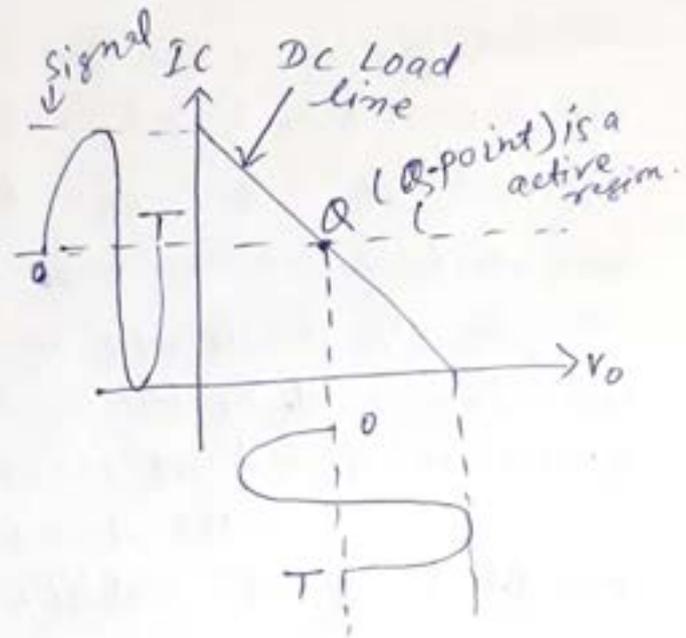
- conduction angle is  $0 - 2\pi$
- Less efficiency
- Distortion is more
- ckt is simple.



The class A amplifier is acting in active region at Q point.  
(First step is a A class amplifier).

⇒ CLASS B Amplifier:

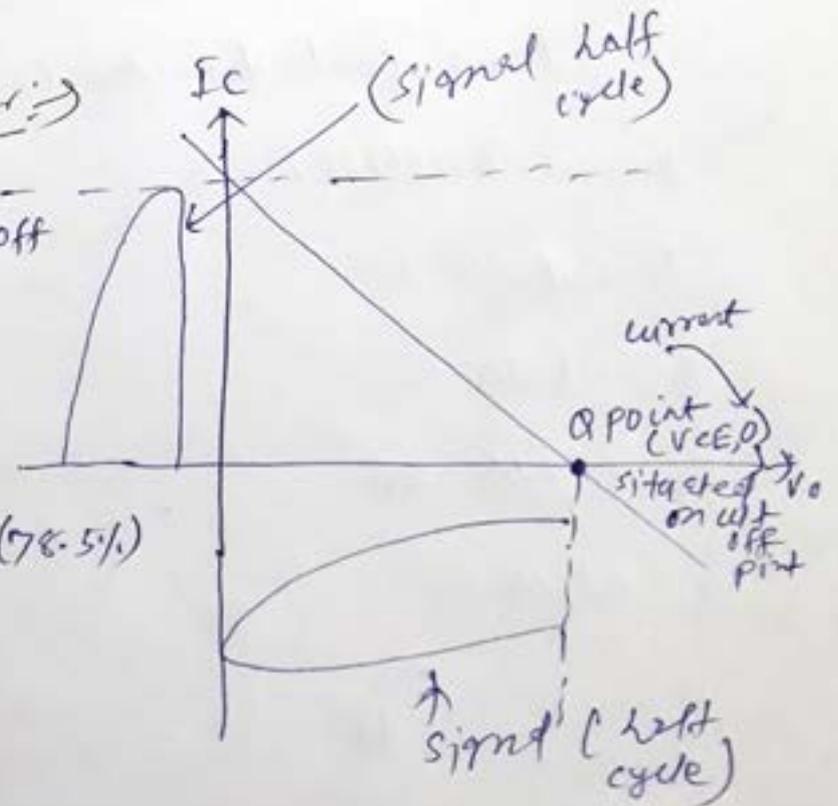
- Q point on cut-off region
- Conduction angle  $0 - 180^\circ$
- High efficiency (78.5%)
- Exp: - ckt.



This is called ckt. ⇓

Exp:- ckt

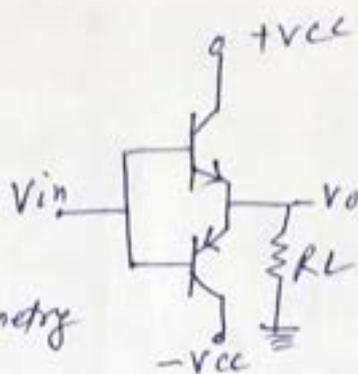This is called Complementary symmetry power amplifier.




(Two transistors  
NPN & PNP)  
d


Use:- Used in o/p stages of class audio system amplifier.

⇒ Class AB Amplifier:-

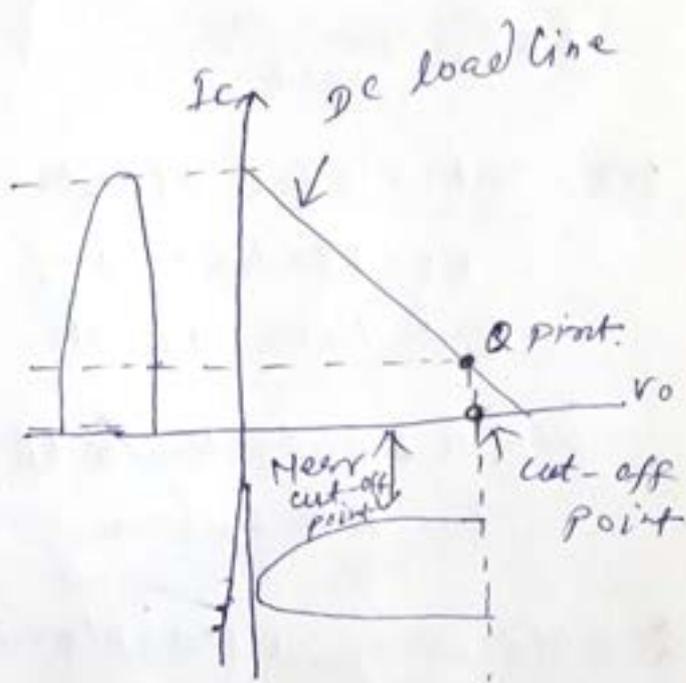- Q point is just above cut-off & just below Active region.
- Conduction angle  $180^\circ - 360^\circ$
- Crossover distortion




Exp:- ckt

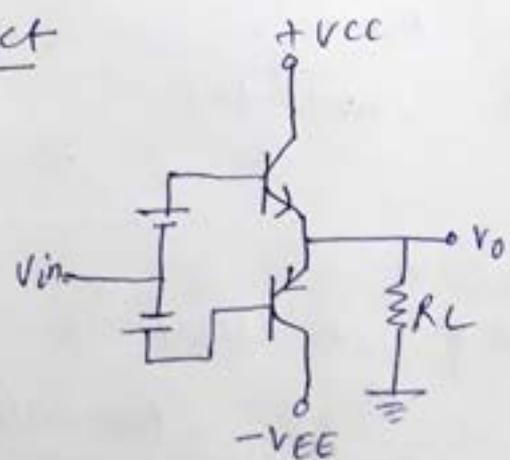

Use:- output (o/p) stage of audio power amplifier.

⇒ Class-C ⇒

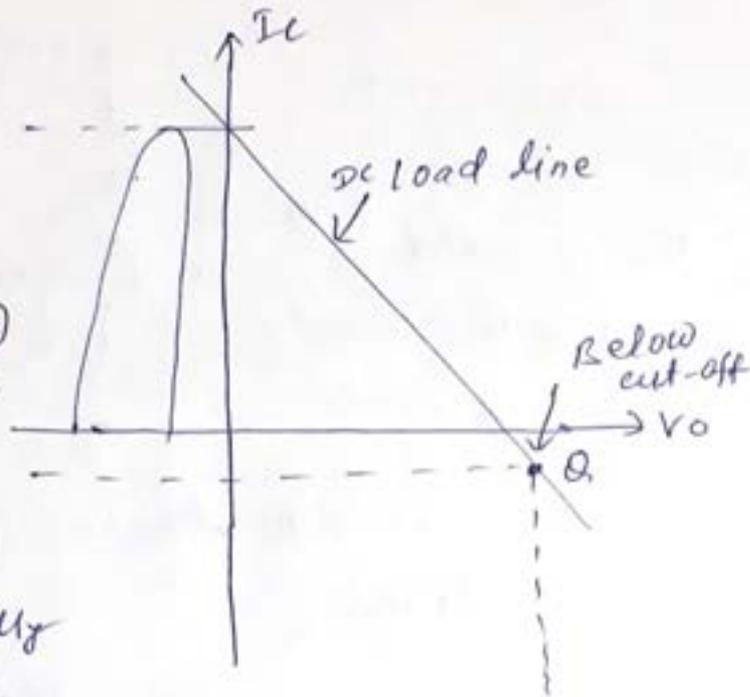- Q point below cut-off region
- Increase in efficiency (> 90%)
- Distortion is high
- Less conduction <math>< 180^\circ</math> (<math>< 100^\circ</math>)
- [60°] is generally used.



⊖:- Ckt is formed with  
RFC (Radio frequency choke)  
and Tank circuit.

Vse ⇒ RF system output stage  
RF System.

\* Efficiency ⇒ (Applied DC power)

$$\text{Efficiency} = \frac{P_{ac}}{P_{dc}} = \frac{\text{Power ac}}{\text{Power dc}}$$

Viva Ques

Power <sup>amplifier</sup> efficiency gives efficiency  

$$= \frac{P_{oac}}{P_{indc}} = \frac{\text{Power out ac}}{\text{Power in dc}}$$

Power eff <math>< 100\%</math>