

Unit -> 1 Diode Circuits  
Subject -> Analog Circuits  
Faculty -> Dr Nidhi chauhan  
Paper code -> BT 402  
Lecture 5 -> Fet biasing

$$V_{GS2} = 5 - 0 = 5 \text{ V}$$

$T_2$  is nonconducting, OFF (its  $V_T$  is negative), draws only leakage current, offers high resistance ( $R_2$ )

$T_1$  is conducting, ON; offers very low resistance ( $R_1$ ). The circuit equivalent in this state is drawn in Fig. 16.20(b).

**Output**

$$V_o \approx 0 \Rightarrow 0\text{-state}$$

It can be seen from the circuits of Fig. 16.20(b) that

$$V_o = \frac{R_1}{R_1 + R_2} V_{SS} \approx 0 \text{ V}$$

**2. Input**

$$V_i = 0 \text{ V} \Rightarrow 0\text{-state}$$

$$V_{GS2} = -5 \text{ V}, T_2 \text{ conducting (low resistance)}$$

$$V_{GS1} = 0 \text{ V}; T_1 \text{ nonconducting (high resistance)}$$

**Output**

$$V_o \approx 5 \text{ V} \Rightarrow 1\text{-state}$$

We thus see that the circuit acts as an inverter; 1-state input produces 0-state output and 0-state input produces 1-state output.

It is observed in this circuit that only one transistor is turned on in any of the output states. As the transistors are series connected, no current is drawn from the battery source in either of the two states. Current is drawn from the battery only during state transition (either way). CMOS circuits, therefore, draw extremely low power from the battery source and so their energy consumption is very small. This is the major attraction why CMOS is used in digital applications.

**16.6 FET BIASING**

We shall consider only voltage-divider biasing as this is most commonly adopted. By examining the drain characteristics of the device, a  $Q$ -point is selected in the middle of the saturation region, which fixes  $V_{GSQ}$  and  $I_{DQ}$ . The biasing circuit resistors are to be selected for the device under dc conditions to operate at the  $Q$ -point.

**16.6.1 Voltage Divider Biasing**

The circuit is drawn in Fig. 16.21. It is the same for any FET.

As per voltage divider

$$V_G = \left( \frac{R_2}{R_1 + R_2} \right) V_{DD} \tag{16.8}$$

Then

$$V_{GS} = V_G - I_D R_S, I_S = I_D \tag{16.9}$$

$I_D R_S$  provides stabilising negative voltage feedback.

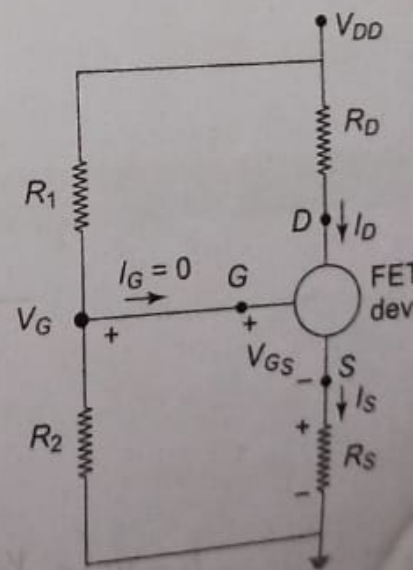


Fig. 16.21

Device transfer characteristic,

$$I_D = f(V_{GS}) \Big|_{\text{Device Parameters}}; \text{nonlinear} \quad (16.10)$$

As  $V_{GSQ}$  has been chosen, the choice of  $R_S$  and simultaneous solution of Eqs (16.8) and (16.9) yields

$I_{DQ}$   
KVL for DS load yields

$$V_{DSQ} = V_{DQ} - I_D(R_S + R_D), R_D \text{ has to be selected} \quad (16.11)$$

Biasing analysis/design is then complete.

### Simultaneous Solution of Eqs. (16.9) and (16.10)

- (i) Equation (16.10) is the transfer characteristic of FET (nonlinear function of  $V_{GS}$ ). Equation (16.9) is a straight line, whose intersection with the transfer characteristic yields  $I_{DQ}$  and  $V_{GSQ}$ .
- or
- (ii) Substituting  $I_D$  from Eq. (16.9) in Eq. (16.10) leads to a quadratic equation in  $V_{GS}$  yielding two solutions from which the appropriate one is to be chosen.

### JFET

Refer Fig. 16.21.

**JFET:**  $I_{DSS} = 10 \text{ mA}$ ,  $V_P = -6 \text{ V}$

**Circuit:**  $R_1 = 2.2 \text{ M}\Omega$ ,  $R_2 = 280 \text{ k}\Omega$ ,  $V_{DD} = 16 \text{ V}$

$R_D = 2 \text{ k}\Omega$ ,  $R_S = 1.5 \text{ k}\Omega$

To determine at Q-point

$V_{GS}$ ,  $I_D$ ,  $V_{DS}$ ,  $V_{DG}$

Plot the transfer characteristic (Fig. 16.22).

 


Fig. 16.22 Transfer characteristic

$$I_D = 10 \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -3 \text{ V}, \frac{V_{GS}}{V_P} = \frac{1}{2}, I_D = 2.5 \text{ mA}$$



$$V_{GS} = 1.5 \text{ V}, \frac{V_{GS}}{V_P} = \frac{1}{4}, I_D = 5.265 \text{ mA}$$

Plot Eq. (16.7).

$$V_G = \frac{280}{2.2 \times 10^3 + 280} \times 16 = 1.8 \text{ V}$$

$$V_{GS} = 1.8 - 1.5 I_D$$

$$I_D = 0, V_{GS} = 1.8 \text{ V}$$

$$V_{GS} = 0, I_D = \frac{1.8}{1.5} = 1.2 \text{ mA}$$

At intersection, Q-point  $\Rightarrow V_{GS} = -2.7 \text{ V}, I_D = 3.1 \text{ mA}$

$$V_{DS} = 16 - (2 + 1.5) \times 3.1 = 5.15 \text{ V}$$

(16.13)

### Analytic Approach

From Eq. (16.13),

$$I_D = \frac{2.8 - V_{GS}}{1.5} = 1.2 - 0.67 V_{GS} \quad (16.14)$$

Substituting  $I_D$  in Eq. (16.13),

$$1.2 - 0.67 V_{GS} = 10 \left( 1 - \frac{V_{GS}}{-6} \right)^2$$

Let  $V_{GS} = x$

$$1.2 - 0.67x = 10 \left( \frac{6+x}{6} \right)^2 = \frac{10}{36} (6+x)^2$$

$$4.32 - 2.41x = x^2 + 12x + 36$$

$$x^2 + 14.41x + 31.68$$

$$x = -2.7, -11.7 \text{ (rejected as more negative than } V_P)$$

Then  $V_{GS} = -2.7 \text{ V}$

The same result as obtained by the graphical solution.

### DMOSFET

Refer Fig. 16.21.

#### DMOSFET parameters

$$I_{DSS} = 8 \text{ mA}, V_P = -4$$

#### Circuit data

$$V_{DD} = 16 \text{ V}$$

$$R_1 = 100 \text{ M}\Omega, R_2 = 10 \text{ M}\Omega,$$

$$R_D = 1.6 \text{ k}\Omega, R_S = 700 \Omega$$

To determine

$$I_{DQ}, V_{GSQ}, V_{DSQ}$$

 


Fig. 16.23 Transfer characteristic

Plotting transfer characteristic (Fig. 16.23),

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -2 \text{ V}; I_D = 8 \left( 1 - \frac{1}{2} \right)^2 = 2 \text{ mA}$$

$$V_{GS} = -1 \text{ V}, I_D = 8 \left( 1 - \frac{1}{4} \right)^2 = 4.5 \text{ mA}$$

$$V_{GS} = +1 \text{ V}, I_D = 8 \left( 1 - \frac{1}{4} \right)^2 = 12.5 \text{ mA}$$

Plotting Eq. (16.8),

$$V_G = \frac{10}{100 + 10} \times 16 = 1.45 \text{ V}$$

$$V_{GS} = V_G - 0.7 I_D$$

$$I_D = 0 \quad V_{GS} = V_G = 1.45 \text{ V}$$

$$V_{GS} = 0 \quad I_D = \frac{1.45}{0.7} = 2.07 \text{ mA}$$

At intersection, Q-point

$$I_{DQ} = 3.8 \text{ mA}, V_{GSQ} = -1.2 \text{ V}$$

From Eq. (16.10),

$$V_{DSQ} = 16 - (1.6 + 0.7) \times 3.8 = 7.26 \text{ V}$$

Refer Fig. 16.21.

## EMOSFET parameters

$$V_T = 4 \text{ V}, V_{GS(\text{on})} = 8 \text{ V}, I_{D(\text{on})} = 2.5 \text{ mA}$$

## Biasing circuit

$$V_{DD} = 35 \text{ V}, R_1 = 20 \text{ M}\Omega, R_2 = 16 \text{ M}\Omega$$

$$R_D = 2.5 \text{ k}\Omega, R_S = 0.75 \text{ k}\Omega$$

To determine: At Q-point

$$I_{DQ}, V_{GSQ}, V_{DS}$$

Plot transfer characteristic (Fig. 16.24).

 


Fig. 16.24

$$k = \frac{2.5}{(8 - 4)^2} = 0.156 \text{ mA/V}^2$$

$$I_D = 0.156 (V_{DS} - 4)^2$$

$$V_{GS} = 8 \text{ V}, I_D = 0.156 \times 16 = 2.5 \text{ mA}$$

$$V_{GS} = 12 \text{ V}, I_D = 0.156 \times 64 = 10 \text{ mA}$$

Plot Eq. (16.8).

$$V_G = \frac{16}{20 + 16} \times 35 = 15.55 \text{ V}$$

$$V_{GS} = 15.55 - 0.75 I_D$$

$$V_{GS} = 0, I_D = 20.7 \text{ mA}$$

$$I_D = 0, V_{GS} = 15.55$$

At Q-point,

$$V_{GSQ} = 9.2 \text{ V}, I_{DQ} = 8.4 \text{ mA}$$





AI QUAD CAMERA  
REDMI NOTE 8 PRO

From Eq. (16.11),

$$V_{DS} = 35 - (2.5 + 0.7) \times 8.4 = 8.12 \text{ V}$$

**n-channel JFET**

Refer Fig. 16.21 directions of  $I_D$  and  $I_S$  reverse,  $V_{DD}$  is negative, JFET parameters  $I_{DSS} = 10 \text{ mA}$ ,  $V_P = 6 \text{ V}$  (positive).

**Biasing circuit**

$$V_{DD} = -20 \text{ V}, R_1 = 64 \text{ k}\Omega, R_2 = 20 \text{ k}\Omega$$

$$R_D = 2 \text{ k}\Omega, R_S = 1.2 \text{ k}\Omega$$

**To determine at Q-point**

$$V_{GSQ}, I_{DQ}, V_{DS}$$

**Shockley's equation**

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$I_D = 10 \left( 1 - \frac{V_{GS}}{6} \right)^2$$

**Voltage divider**

$$V_G = \frac{20}{64 + 20} \times (-20) = -4.76 \text{ V}$$

**KVL for GS loop (adjoining Fig. 16.25)**

$$V_G - V_{GS} + R_S I_D = 0; I_D = I_S; \text{ direction of currents } S \text{ to } D$$

$$-4.76 - V_{GS} + 1.2 I_D = 0; I_D = I_S$$

or

$$I_D = \frac{4.76 + V_{GS}}{1.2} = 4 + 0.833 V_{GS}$$

Let

$$V_{GS} = x,$$

Substituting  $I_D$  in Eq (16.15),

$$4 + 0.833x = \frac{10}{36} (6 - x)^2$$

$$14.4 + 3x = 36 - 12x + x^2$$

$$x^2 - 15x + 21.6 = 0 \Rightarrow x = 1.6 \text{ V}, 13.476 \text{ V (rejected)}$$

Then,

$$V_{GSQ} = 1.6 \text{ V}$$

$$I_{DQ} = 10 \left( 1 - \frac{1.6}{6} \right)^2 = 5.38 \text{ mA}$$

**KVL DS loop,**

$$-20 - (2 + 1.2) \times 5.38 - V_{DS} = 0$$

or

$$V_{DS} = -2.78 \text{ V}$$

 


Fig. 16.25

(16.15)