

~~Barkhausen~~

## Barkhausen criteria



1. An oscillator will operate at high frequency for which the total phase shift introduced, as measured from the input terminals, through the amplifier and feedback network and back again to the input is precisely equal to 0 or 360° or integral multiple of 360°.
2. At the oscillator frequency, the magnitude of the product of open loop gain of the amplifier 'A' and the feedback factor (B) is greater than unity.

$$\therefore |AB| \gg 1.$$

A → voltage gain  
B → feedback factor.

LC (Inductor-Capacitor) Oscillator.

(1). HARTLEY OSCILLATOR :->

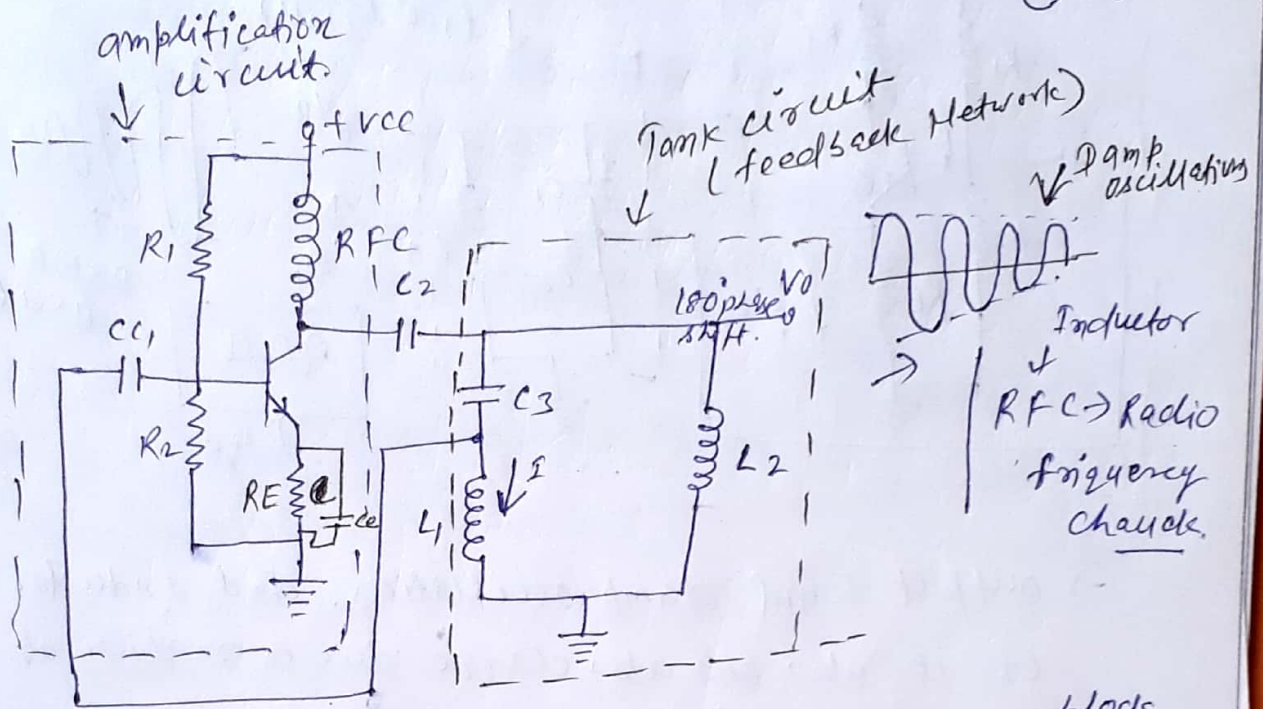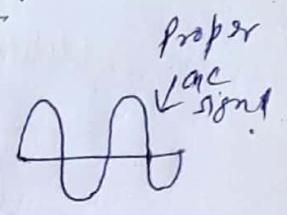

RFC (Radio frequency choke) is a ac signal ~~pass~~ <sup>block</sup> and dc signal ~~pass~~ in circuit. the capacitor C2 is charge with +vcc, similarly C3 is also charge.

- > Capacitor not pass d.c. signal. only pass ac signal.
- > Inductor as a magnetic field charge stored.

We found as ~~sin~~ ac signal (like) not a damp ~~oscillation~~, BJT is a amplify the signal and repeat it.

$$f = \frac{1}{2\pi \sqrt{C_3(L_1+L_2)}} = \frac{1}{2\pi \sqrt{C_3 L_{eq}}}$$

$L_{eq}$  -> Inductor equivalent.  
 $L$  -> Inductor.  
 $C$  -> capacitor

$L_1$  &  $L_2$  are in series.