

where

$L_1$  = self inductance of coil 1

$L_2$  = self inductance of coil 2

$N_1$  = Number of turns of coil 1

$N_2$  = Number of turns of coil 2

$\phi_1$  = magnetic flux emanating from coil 1

$\phi_{11}$  = one component of  $\phi_1$ , has coil 1 only

$\phi_{12}$  = another component of  $\phi_1$  links both coil 1 and coil 2.

Hence

$$\phi_1 = \phi_{11} + \phi_{12}$$

Although the two coils are physically separated, they are said to be magnetically coupled.

Since the entire flux  $\phi_1$  links coil 1, the voltage induced in coil 1 is,

$$V_1 = N_1 \frac{d\phi_1}{dt}$$

September '11

Monday	5	12	19	26
Tuesday	6	13	20	27
Wednesday	7	14	21	28
Thursday	1	8	15	22
Friday	2	9	16	23
Saturday	3	10	17	24
Sunday	4	11	18	25

Notes

Appointment

Only flux  $\phi_{12}$  links coil 2, so that voltage induced in coil 2 is

$$V_2 = N_2 \frac{d\phi_{12}}{dt}$$

Again, as the fluxes are caused by the current  $i_1$ , flowing in coil 1, we can

write

$$V_1 = N_1 \frac{d\phi_1}{di_1} \cdot \frac{di_1}{dt} = L_1 \frac{di_1}{dt}$$

where

$$L_1 = N_1 \frac{d\phi_1}{di_1} = \text{self-inductance of coil 1}$$

similarly

$$V_2 = N_2 \cdot \frac{d\phi_{12}}{di_1} \cdot \frac{di_1}{dt} = M_{21} \cdot \frac{di_1}{dt}$$

$$\text{where } M_{21} = N_2 \cdot \frac{d\phi_{12}}{di_1}$$

$M_{21}$  = mutual inductance of coil 2 with respect to coil 1

Subscript 21 indicates that inductance  $M_{21}$  relates the voltage induced in coil 2 to the current in coil 1.

	31	3	10	17	24
Monday		4	11	18	25
Tuesday	5	12	19	26	
Wednesday	6	13	20	27	
Thursday	7	14	21	28	
Friday	1	8	15	22	29
Saturday	2	9	16	23	30
Sunday					



Thus the open ckt- mutual voltage (or induced voltage) across coil 2 is

$$V_2 = M_{21} \frac{di_1}{dt}$$

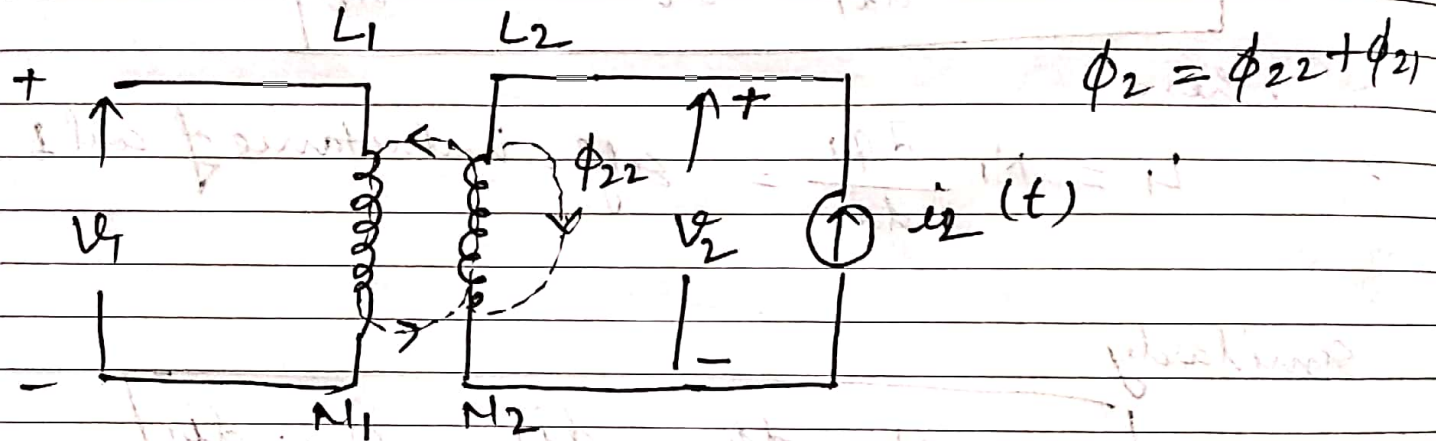


fig: Mutual inductance  $M_{12}$  of coil 1 with respect to coil 2.

summary

$$\phi_2 = \phi_{21} + \phi_{22}$$

$$V_2 = N_2 \frac{d\phi_2}{dt} = \left( N_2 \frac{d\phi_2}{di_2} \right) \frac{di_2}{dt} = L_2 \frac{di_2}{dt}$$

$$V_1 = N_1 \frac{d\phi_{21}}{dt} = \left( N_1 \frac{d\phi_{21}}{di_2} \right) \frac{di_2}{dt} = M_{12} \frac{di_2}{dt}$$

September 11				
Monday	5	12	19	26
Tuesday	6	13	20	27
Wednesday	7	14	21	28
Thursday	1	8	15	22
Friday	2	9	16	23
Saturday	3	10	17	24
Sunday	4	11	18	25

Notes

Appointment

$$V_1 = M_{12} \frac{di_2}{dt}$$



$M_{12}$  and  $M_{21}$  are equal, that is Day (265-100) • Week 49

$$M_{12} = M_{21} = M$$

Keep in mind that mutual coupling only exists when the inductors or coils are in close proximity, and the circuits are driven by time varying sources.  
Recall that inductors act like short-circuit to DC.

The polarity of mutual voltage ( $M \frac{di}{dt}$ ) is not easy to determine, because four terminals are involved.

The choice of the correct polarity for  $M \frac{di}{dt}$  is made by examining the orientation or particular way in which both coils are physically wound and applying Lenz's law in conjunction with the right-hand rule.

We will apply the dot convention in circuit analysis.

By this convention, a dot is placed in the circuit at one end of each of the two magnetically coupled coils to indicate the direction of the magnetic flux if current enters that dotted terminal of the coil.

October '11

Notes	Appointment	Monday	31	3	10	17	24
		Tuesday		4	11	18	25
		Wednesday		5	12	19	26
		Thursday		6	13	20	27
		Friday		7	14	21	28
		Saturday		1	8	15	22
		Sunday		9	16	23	30