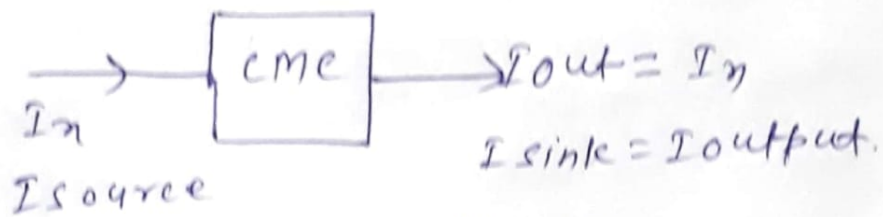


UNIT-IV


Current mirror circuit.

The circuit is force to output ^{current} signal is equal to input current. that is output current is mirror image of input current. This is known current mirror circuit.



Block diagram.

Concept.

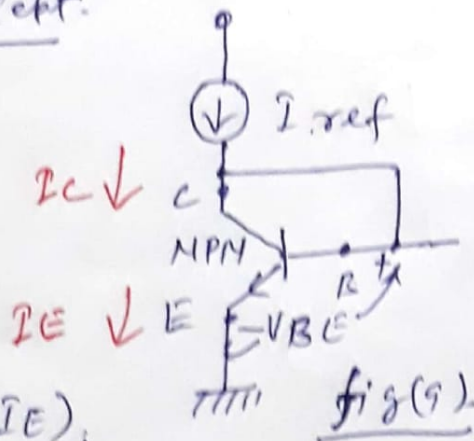

$(I_C = I_E)$,

if $\beta = \text{large} = \infty$, then

$$I_B = 0A$$

$$I_C = I_E$$

Now, Emitter current (I_E),

$$I_E = I_0 e^{V_{BE}/V_T}$$

Where, $V_T \rightarrow \frac{T}{11600} \rightarrow$ Thermal voltage.

$I_0 \rightarrow$ Reverse saturation current (R.S.C).

$$\left. \begin{aligned} V_{CB} &= V_C - V_B \\ V_{CB} &= 0 \text{ Volts} \end{aligned} \right\} \begin{aligned} V_C \text{ \& } V_B \\ &\text{are same} \\ &\text{so} \\ &V_{CB} = 0V \end{aligned}$$

This figure is known as diode connected transistor.

$I_{ref} \rightarrow$ Reference current.

if $I_E = I_C = I_{ref}$, then,

$$I_{ref} = I_0 e^{V_{BE1}/V_T}$$

$$\frac{I_{ref}}{I_0} = e^{V_{BE1}/V_T}$$

Taking log natural both side, then

$$\ln \frac{I_{ref}}{I_0} = \frac{V_{BE1}}{V_T}$$


$$\therefore \boxed{V_{BE1} = V_T \ln \left(\frac{I_{ref}}{I_0} \right)} \quad \text{--- (1)}$$

Now, fig(b).

if $I_C = I_E = I_{out}$

$$= I_0 e^{V_{BE2}/V_T}$$

Similar to above eqⁿ.

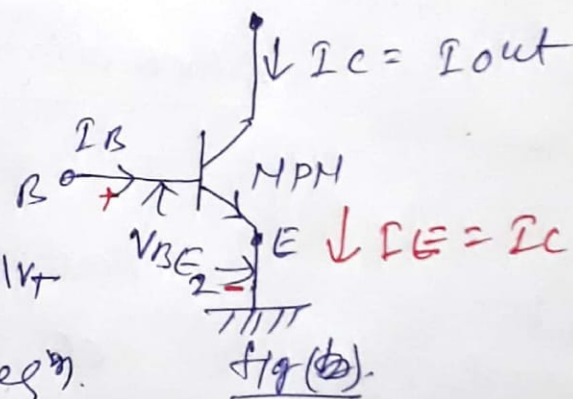

$$\boxed{V_{BE2} = V_T \ln \left(\frac{I_{out}}{I_0} \right)} \quad \text{--- (2)}$$

if $V_{BE1} = V_{BE2}$, then


$$V_T \ln \frac{I_{ref}}{I_0} = V_T \ln \frac{I_{out}}{I_0}$$

$$\ln \frac{I_{ref}}{I_0} = \ln \frac{I_{out}}{I_0}$$

$$\therefore \boxed{I_{ref} = I_{out}} \quad \text{---}$$

⇓

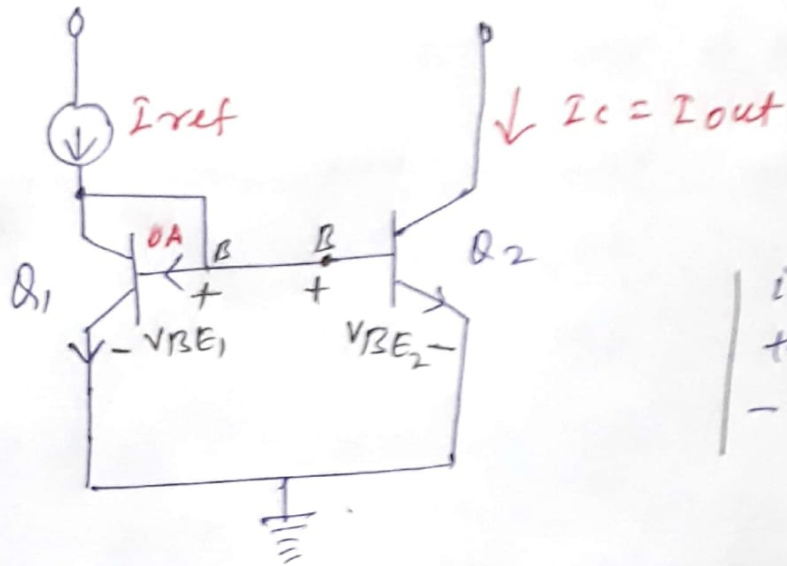① If both transistors voltage ($V_{BE1} = V_{BE2}$) Then,



if Apply KVL
then,
 $-V_{BE1} + V_{BE2} = 0$

fig 10. Basic current mirror ckt.

if suppose $\beta \neq \infty$, then


$$I_B \neq 0A$$

so,

$$I_{ref} = I_C + 2I_B$$

$$= I_C + 2\left(\frac{I_C}{\beta}\right)$$
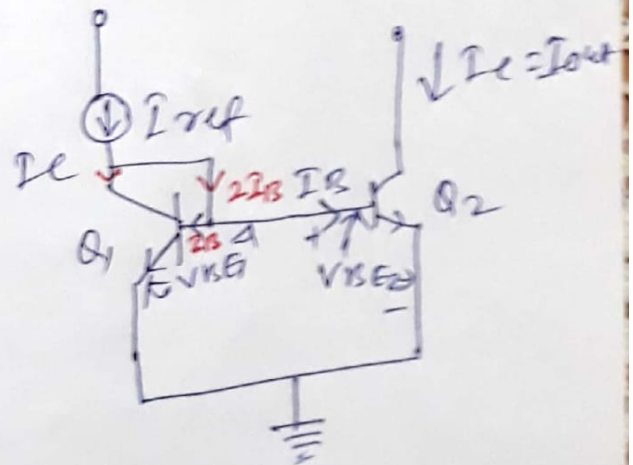
$$I_{ref} = I_C \left[\frac{\beta + 2}{\beta} \right]$$



$$I_{ref} = I_{out} \left[\frac{\beta + 2}{\beta} \right]$$

$$\therefore I_{out} = I_{ref} \left[\frac{\beta}{\beta + 2} \right]$$

(2). Requirement for current mirror circuit is

(Both transistor are identical & same.)

1. ~~R_{BE}~~ $V_{BE1} = V_{BE2} = V_{BE}$
2. $I_{C1} = I_{C2} = I_C$
3. $I_{B1} = I_{B2} = I_B$
4. $\beta_1 = \beta_2 = \beta$ (large)

(3) Junction Area's (AE). (~~Area~~)

$$AE_1 = AE_2 \quad \checkmark$$

$$AE \propto I_0 \quad \checkmark$$

\Rightarrow if let, $AE_2 = 2AE_1$

$$I_{O2} = I_{O1}$$

$$V_{BE2} = V_T \ln \frac{I_{out}}{I_{O2}}$$

$$V_{BE1} = V_T \ln \frac{I_{out}}{I_{O1}}$$

V.V.E. \rightarrow $I_{out} = 2I_{ref}$ \checkmark


$AE \rightarrow$ junction Area.

$$\frac{I_{out}}{I_{O2}} = \frac{I_{ref}}{I_{O1}}$$

$$\frac{I_{out}}{2I_{O1}} = \frac{I_{ref}}{I_{O1}}$$

$$I_{out} = 2I_{ref}$$

① →

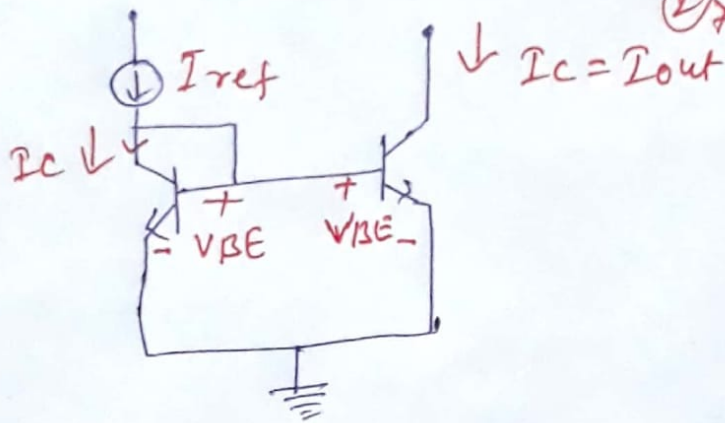


fig(a)-

$$I_{out} = \left(\frac{\beta}{\beta + 2} \right) I_{ref}$$

$$I_{out} = I_{ref} \quad (\beta = \infty)$$

u

② →

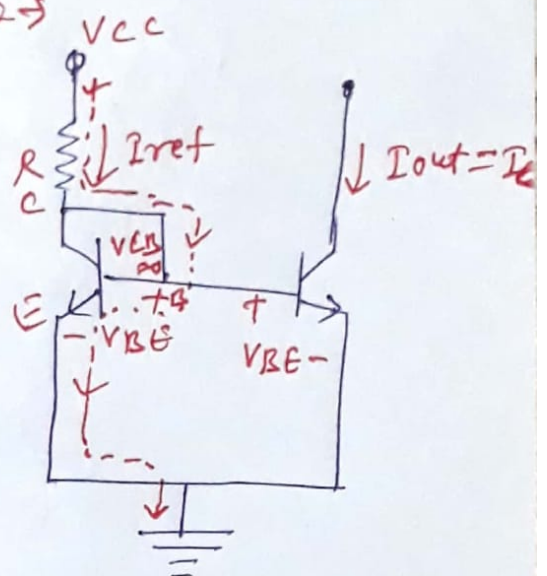

fig(b)-

$$I_{out} = \left(\frac{\beta}{\beta + 2} \right) I_{ref}$$


$$I_{out} = I_{ref} \quad (\beta = \infty)$$

Now Apply KVL, then

$$V_{CC} = I_{ref} \cdot R + 0 + V_{CE}$$

$$\therefore I_{ref} = \frac{V_{CC} - V_{CE}}{R}$$

③ →

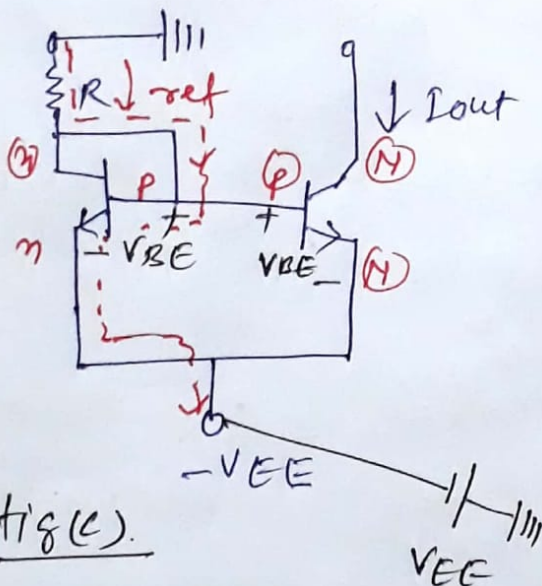

fig(c)-

$$I_{out} = \left(\frac{\beta}{\beta + 2} \right) I_{ref}$$


$$I_{out} = I_{ref} \quad (\beta = \infty)$$

Apply KVL,

$$0 + I_{ref} \cdot R + 0 + V_{BE} - V_{EE}$$

$$\therefore I_{ref} = \frac{V_{BE} - V_{EE}}{R}$$

④

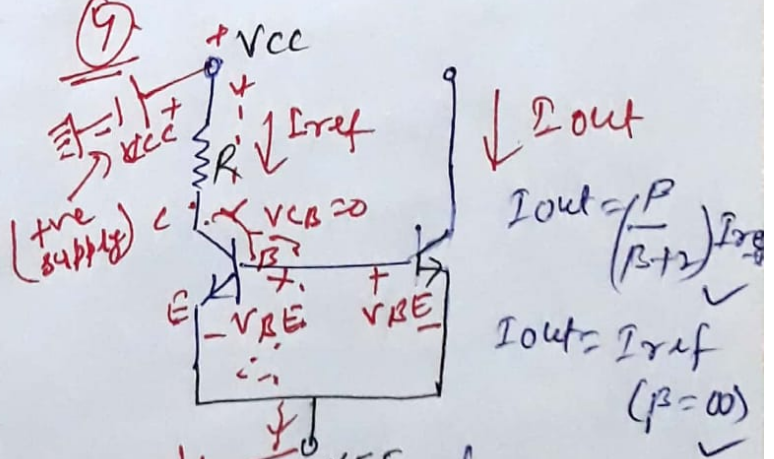


fig(d)

$$V_{CC} = I_{ref} \cdot R + 0 + V_{BE} - V_{EE}$$

$$\therefore I_{ref} = \frac{V_{CC} + V_{BE} + V_{EE}}{R}$$

5

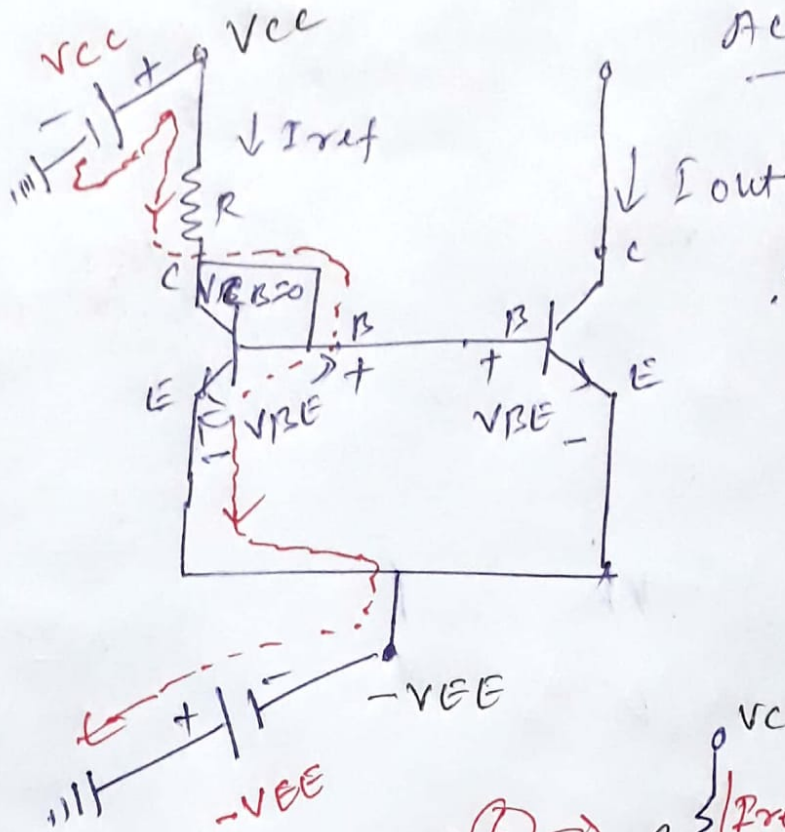

According to ohm's law:

$$-V_{CC} + I_{ref} \cdot R + V_{BE} - V_{EE} = 0$$

$$\therefore I_{ref} = \frac{V_{CC} - V_{BE} + V_{EE}}{R}$$

$I_{out} \approx I_{ref}$ (log Match)

* $\Rightarrow I_{out} = I_{ref}$

$I_{out} \approx I_{ref}$ (small)


$I_{ref} = \text{small}$

$R \rightarrow \text{large}$

chip Area of R

chip Area \rightarrow large

6

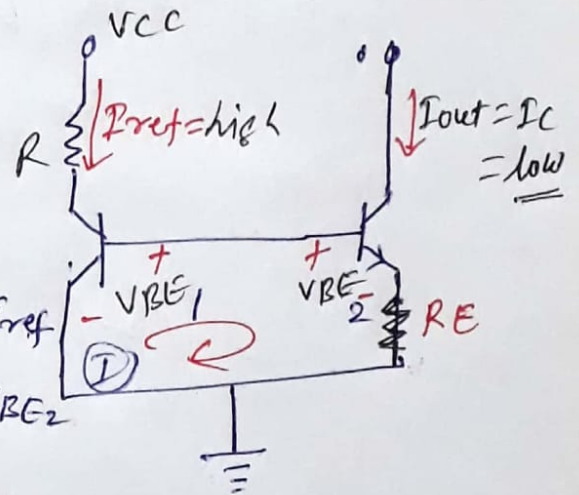

$I_{out} \neq I_{ref}$

$V_{BE1} \neq V_{BE2}$

According to Widlar's circuit:

$I_{out} = I_{ref}$ ✓

$I_{out} = \text{low}$ ✓

$I_{ref} = \text{high}$ ✓

Widlar current mirror ckt. (Widlar ckt.)

(The Widlar ckt is used to input current high & output current low)

$V_{BE1} = V_T \ln \frac{I_{ref}}{I_0}$

$V_{BE2} = V_T \ln \frac{I_{out}}{I_0}$

Now, apply KVL in

$-V_{BE1} + V_{BE2} + I_{out} RE = 0$

$\therefore I_{out} RE = V_{BE1} - V_{BE2}$

$I_{out} RE = V_{BE1} - V_{BE2}$

$I_{out} RE = V_T \ln \frac{I_{ref}}{I_0} - V_T \ln \frac{I_{out}}{I_0}$

$I_{out} RE = V_T \ln \left[\frac{I_{ref}}{I_{out}} \right]$ (log x - log y = log x/y)

$RE = \frac{V_T}{I_{out}} \ln \left[\frac{I_{ref}}{I_{out}} \right]$ ✓