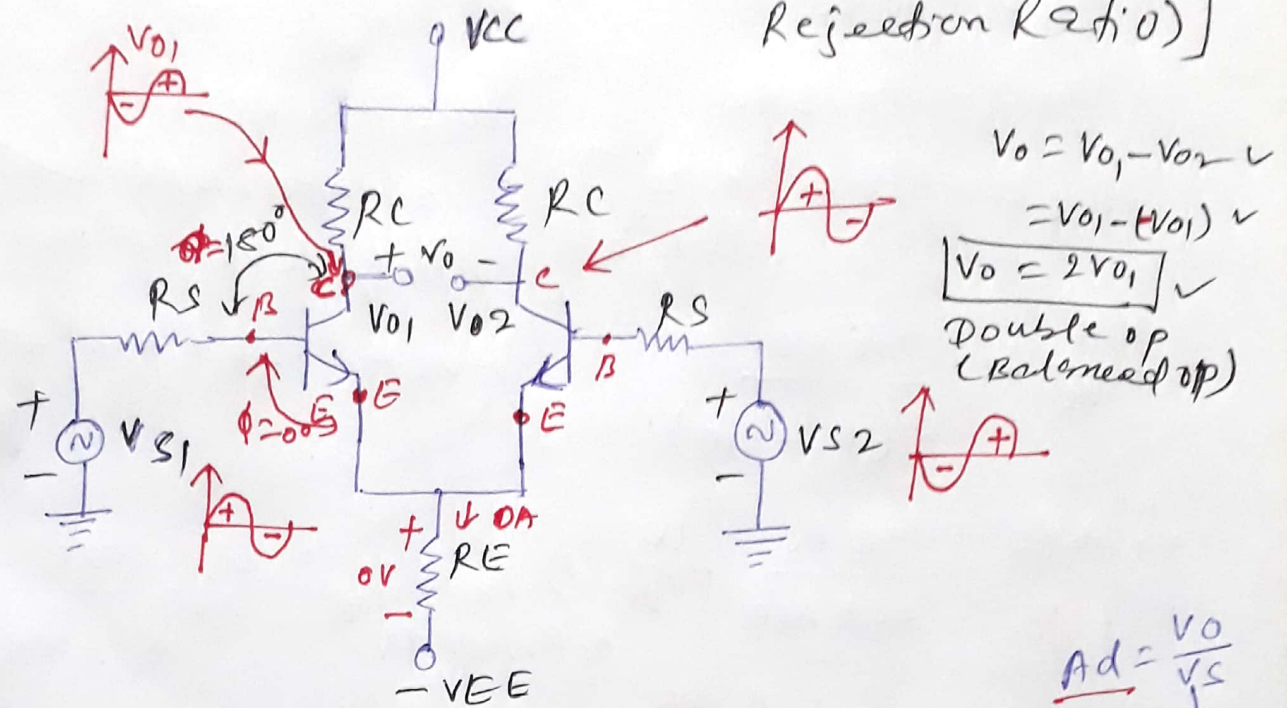


AC Analysis (that is Amplifier Analysis)

[Calculation of $CMRR$ (common mode Rejection Ratio)]



$$V_O = V_{O1} - V_{O2}$$

$$= V_{O1} - (-V_{O1})$$

$$\boxed{V_O = 2V_{O1}}$$

Double op (Balanced op)

fig (differential Amp^r)

AC analysis is have two modes:-

$$CMRR = \left| \frac{A_d}{A_c} \right| = \dots$$

where,

$|A_d|$ = magnitude of diff. mode gain

$|A_c|$ = " " common mode gain

$$V_d = V_{S1} - V_{S2} = \frac{V_S}{2} - \left(-\frac{V_S}{2}\right) = V_S$$


$$V_c = \frac{V_{S1} + V_{S2}}{2} = \frac{V_S + V_S}{2} = V_S$$

$$A_d = \frac{V_O}{V_S}$$

$\phi = 180^\circ$

Hybride model of diff. Amp^r (1st part)
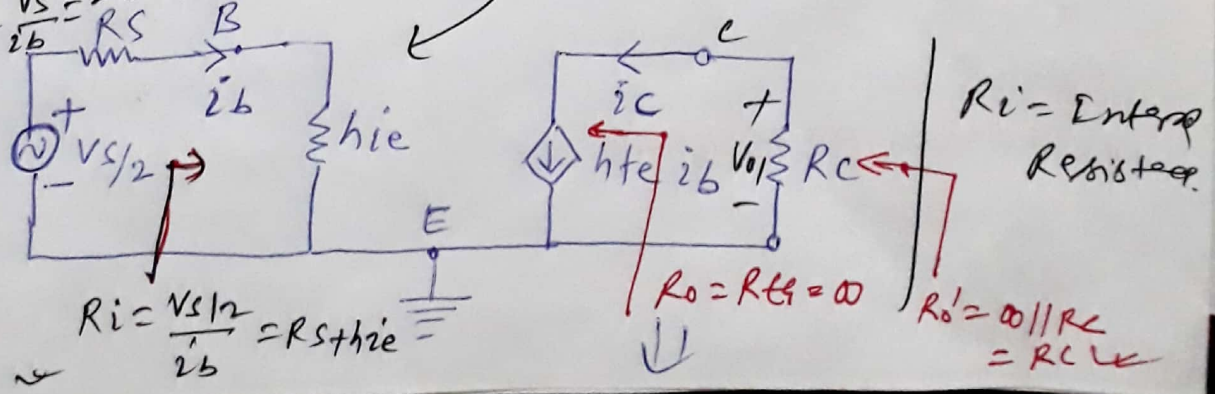
$$R_i \text{ [D. Amp]} = \frac{V_S}{i_B} = 2(R_S + h_{ie})$$



$$A_c = \frac{V_{O1}}{V_S}$$

R_i = Input Resistance

$$A_d = \frac{V_o}{V_s} = \frac{2V_{o1}}{V_s}$$

$$V_{o1} = -i_c R_C$$

$$V_{o1} = -h_f e_{i_b} R_C$$

$$V_{o1} = -h_f e R_C \left[\frac{V_s/2}{R_s + h_{ie}} \right]$$

$$\frac{V_{o1}}{V_s} = \frac{-h_f e R_C}{2(R_s + h_{ie})}$$

$$\therefore A_d = \frac{-h_f e R_C}{R_s + h_{ie}}$$

↑
Differential gain

$$A_d = \frac{-\beta R_C}{R_s + r_{\pi}}$$

In form of
re model.

if $R_s \ll r_{\pi}$, then

$$A_d = \frac{-\beta R_C}{r_{\pi}} = -g_m R_C$$

Ans.

$$V_o = V_{o1} - V_{o2}$$

$$V_o = 0$$

In common mode gain,
Balance o/p \Rightarrow
Unbalance o/p
single o/p, \checkmark
 V_{o1} .

Common mode gain

$$A_c = \frac{V_{o1}}{V_s}$$

$$V_{o1} = -i_c R_C$$

$$= -h_f e_{i_b} R_C$$

Apply KVL, then

$$-V_s + R_s i_b + h_{ie} i_b + 2R_E (1+\beta) i_b = 0$$

$$i_b = \frac{V_s}{R_s + h_{ie} + 2R_E(1+\beta)}$$

$$A_c = \frac{V_{o1}}{V_s} = \frac{-h_f e R_C}{R_s + h_{ie} + 2R_E(1+\beta)}$$

$$= \frac{-\beta R_C}{R_s + r_{\pi} + 2R_E(1+\beta)}$$

$$S = \left| \frac{A_d}{A_c} \right| = \frac{R_s + h_{ie} + 2R_E(1+\beta)}{R_s + r_{\pi}}$$

$$S = \frac{R_s + r_{\pi} + 2R_E(1+\beta)}{R_s + r_{\pi}}$$

if $R_s \ll r_{\pi}$,

$$S = \frac{r_{\pi} + 2R_E(1+\beta)}{r_{\pi}}$$

V.V.I

	RE	Ad	Ac	ϕ
\uparrow		NC	\downarrow	\uparrow
\downarrow		NC	\uparrow	\downarrow

✓

NC \rightarrow No change.

$$\phi = \frac{g_{m} R_{E}}{r_{e}}$$

$$g_{m} = \frac{I_{c}}{V_{T}} \quad \frac{V.V.I}{\checkmark}$$