

Department of ECE

Name of faculty: → Er. Vijay Kr. Ram

Subject: - Analog Circuit.


(EC - 2nd yr, 4th sem.)

Query Time: → 03:00 PM - 04:00 PM.


Wien Bridge Oscillator (RC oscillator) (64)

- A Wien bridge oscillator is an electronic oscillator that generates sine waves.
- it is developed by Max Wien in 1891 for the measurement of impedance.
- This oscillator is also an RC oscillator which uses Wien Wien bridge circuit as a feedback network.
- The bridge circuit does not introduce any phase shift, or 0° phase shift.
- The bridge ckt consists four resistors & two capacitors.
- Therefore, the amplifier that we are using in this oscillator is non-inverting amplifier which does not introduce any phase shift.

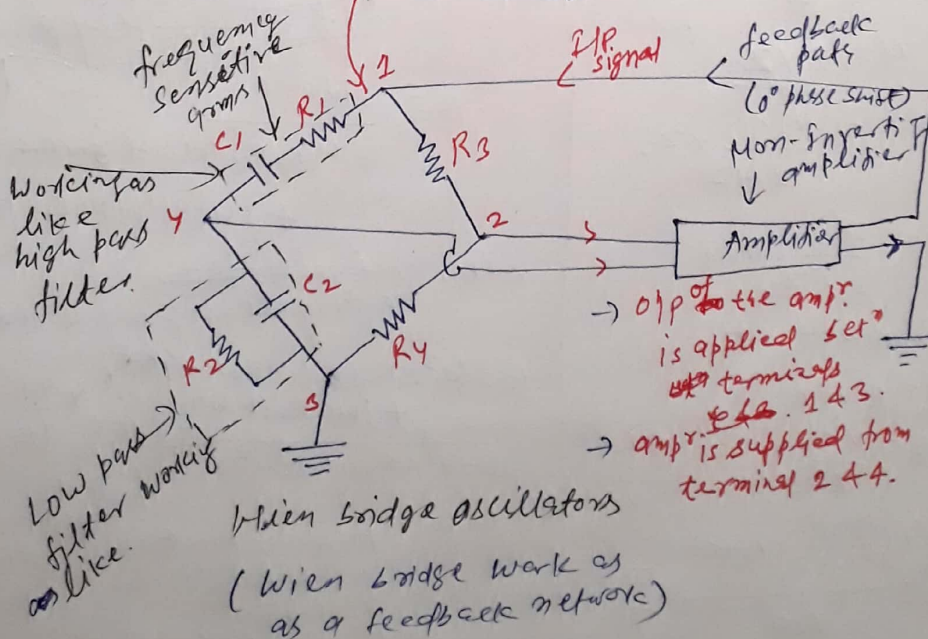Wien bridge → feedback net
det 0° or 360°



Lead-Lag Network

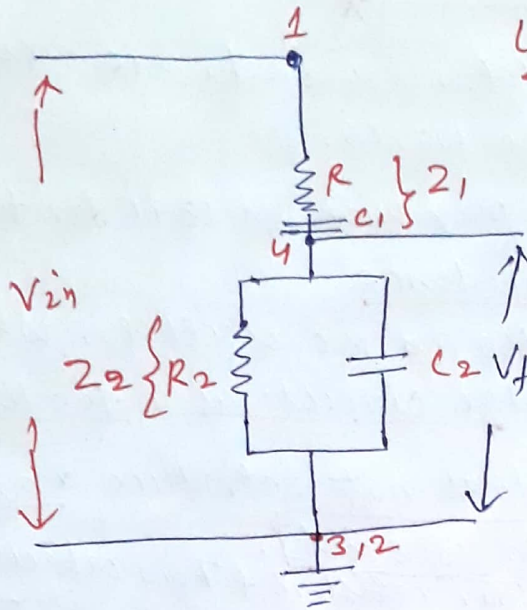

$$Z_1 = R + \frac{1}{j\omega C_1} \quad | \quad Z_1 \rightarrow \text{impedance}$$

$$Z_1 = \frac{1 + j\omega R C_1}{j\omega C_1}$$

$$Z_2 = \frac{R_2 \times \frac{1}{j\omega C_2}}{R_2 + \frac{1}{j\omega C_2}} = \frac{R_2}{1 + j\omega R_2 C_2}$$

$$I = \frac{V_{in}}{Z_1 + Z_2} = \frac{V_{in}}{Z}$$

$$V = IR \quad \therefore I = \frac{V}{R} = \frac{V}{Z}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

if $R_1 = R_2 = R$ & $C_1 = C_2 = C$
then

$$f = \frac{1}{2\pi \sqrt{R \cdot R \cdot C \cdot C}}$$

$$f = \frac{1}{2\pi RC} \quad \text{proved}$$

$$\therefore V_f = I \times Z_2$$

$$V_f = \frac{V_{in}}{Z_1 + Z_2} \times Z_2$$

$$V_f = \frac{Z_2}{Z_1 + Z_2} \cdot V_{in}$$

We know that

$$V_f = \beta V_{in}$$

$$\therefore \beta = \frac{V_f}{V_{in}} \quad \left| \quad V_f = \beta V_o \right.$$

$$\beta = \frac{\frac{Z_2}{Z_1 + Z_2} \cdot V_{in}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2}$$

$$\beta = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2}{1 + j\omega R_1 C_1 + \frac{R_2}{1 + j\omega R_2 C_2}}$$

$$\therefore \beta = \frac{j\omega R_2 C_1}{1 - \omega^2 R_1 R_2 C_1 C_2 + j\omega(R_1 C_1 + R_2 C_2 + R_2 C_1)}$$

after rationalization, rationalizing and simplifying

$$\beta = \frac{\omega^2 C_1 R_2 (R_1 C_1 + R_2 C_2 + R_2 C_1) + j\omega C_1 R_2 (1 - \omega^2 R_1 R_2 C_1 C_2)}{(1 - \omega^2 R_1 R_2 C_1 C_2)^2 + \omega^2 (R_1 C_1 + R_2 C_2 + R_2 C_1)^2}$$

for 0° phase, imaginary part = 0, rationalizing form.

$$\omega \neq 0$$

$$4R_2 \omega (1 - \omega^2 R_1 R_2 C_1 C_2) = 0$$

$$\omega (1 - \omega^2 R_1 R_2 C_1 C_2) = 0$$

$$\omega^2 = \frac{1}{R_1 R_2 C_1 C_2}$$

$$\therefore \omega = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \quad \therefore f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$