

Unit -> 2

Subject -> Analog ckt


Faculty -> Dr. Nidhi chauhan

Paper code -> BT-402

Lecture 6 -> Effect of feedback on gain, bandwidth

---

## Effect of feedback on gain

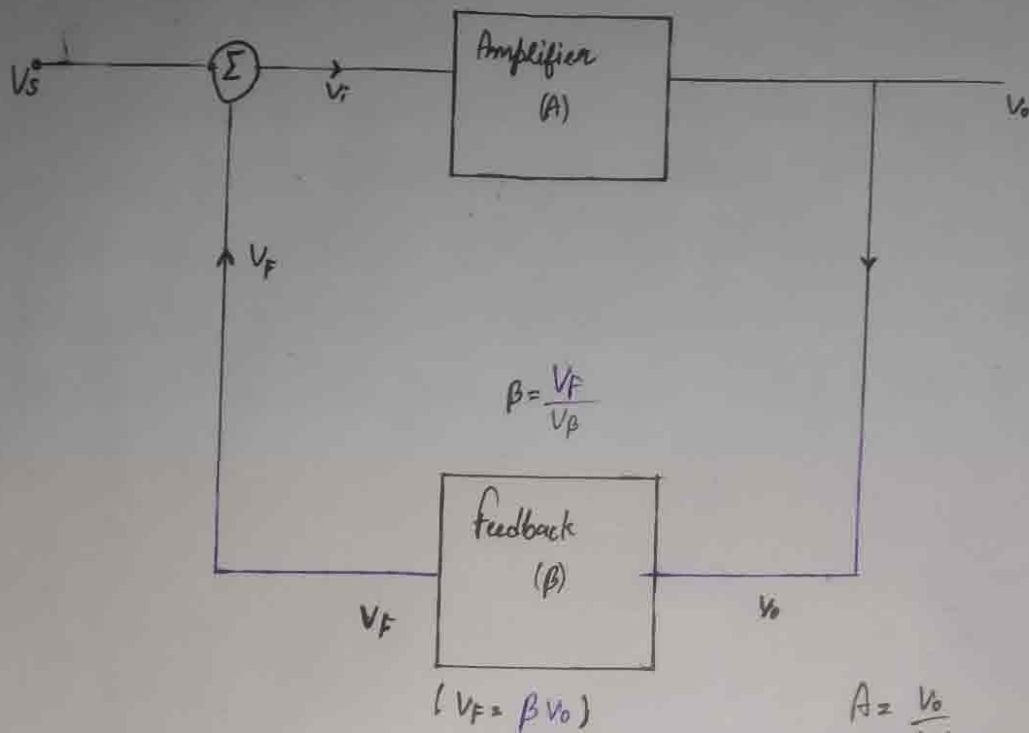

$$\{V_i = V_s \pm V_F\}$$

$$\begin{aligned}V_o &= A V_i \\&= A (V_s \pm V_F) \\&= A (V_s \pm \beta V_o) \\&= A V_s \pm A \beta V_o\end{aligned}$$

$$V_o \mp A \beta V_o = A V_s$$

$$\boxed{\frac{V_o}{V_s} = \frac{A}{1 \mp A\beta} = A_{VF}}$$



## Effect of feedback on bandwidth

The Bandwidth of an amplifier is defined as the range of frequencies for which the gain remains constant. The gain bandwidth product of an Op-amp is always a constant. The gain of an Op-amp and its Bandwidth are Inversely proportional to one another. The Bandwidth of an Op-amp can be increased by providing feedback signal to its Input. The product of closed-loop gain and closed-loop Bandwidth is same as the product of Open-loop gain and open-loop bandwidth. i.e.


$$A_{FBW_{CL}} = A_{BW_{OL}}$$

The Op-amp 741 has Open-loop gain of 200,000 and a bandwidth of about 5Hz. Therefore, the product of its open-loop gain and bandwidth is.

$$A_{BW_{OL}} = 200,000 * 5\text{Hz} = 1\text{MHz}$$

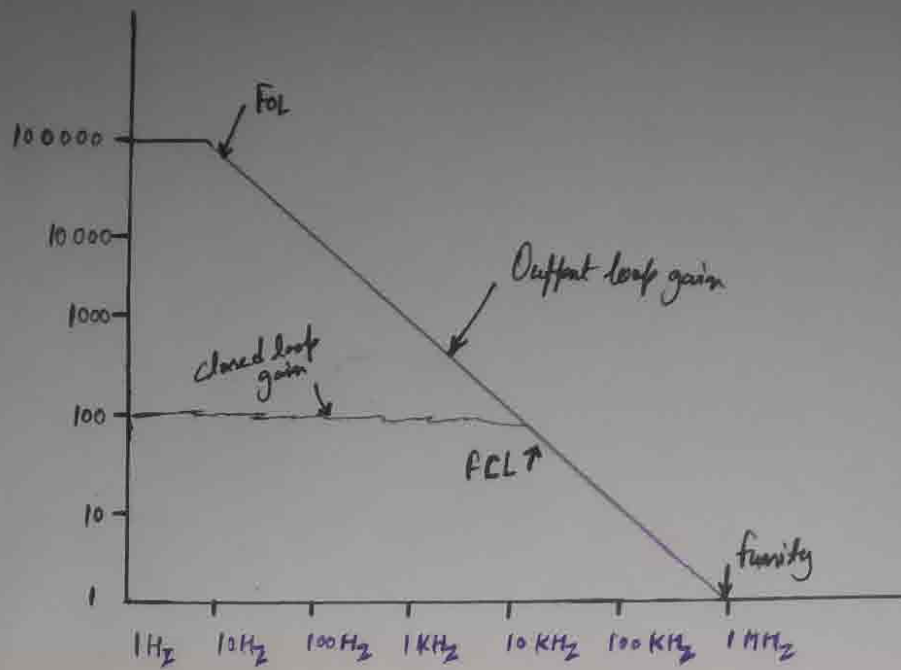The open-loop gain - bandwidth product of 741 is 1MHz. The left-hand side of equation (1) is the product of closed-loop gain and closed-loop bandwidth. No matter what the value of  $R_i$  and  $R_f$ , the product of closed loop gain and closed loop bandwidth must equal the Open-loop gain-bandwidth product, i.e. for 741 the closed-loop gain - bandwidth product must also be 1 MHz.





The open-loop response is shown in fig.

The open-loop gain has a maximum value of 200,000. When the operating frequency increases to 5 Hz, the open-loop gain is down to 0.707 of its maximum value. The gain keeps dropping off with increasing frequency. After the upper cut-off frequency,  $f_{OL}$ , the gain drops by 20 dB/decade.

The unity-gain frequency is the frequency where the open-loop gain has decreased to unity. In figure unity equals 1 MHz.

