

**UNIT-2>>MULTISTAGE AMPLIFIERS**

**CLASS>>II<sub>ND</sub> YEAR, IV SEM**

**SUBJECT-ANALOG CIRCUITS**

**PAPER-CODE>>BT-402**

**LECTURE-NO>>2.8**

**TOPIC>>Cascode Amplifier**

**FACULTY NAME>>DR. NIDHI CHAUHAN**

**CASCODE AMPLIFIER:-**

A common gate emitter stage in cascode with a common source amplifier stage is known as cascode configuration.

The basic idea behind the cascode amplifier is to combine the high input (common-emitter) amplifier with the current buffering property.

It can be design to increase the DC gain while

leaving the gain bandwidth product unchanged.