

UNIT-4 >>CURRENT MIRROR AND OP-AMP DESIGN

CLASS>>II_{ND} YEAR, IV SEM

SUBJECT-ANALOG CIRCUITS

PAPER-CODE>>BT-402

LECTURE-NO>>2.11

TOPIC>>CLASS(A,B,AB,C)Linearity issues

FACULTY NAME>>DR. NIDHI CHAUHAN


Linearity issues of Class A:-

1. An emitter follower (Class A) Q_1 biased with a constant current I supplied by transistor Q_2 .
2. The emitter current $i_{E1} = I + i_L$, the bias current I must be greater than the largest negative load current; otherwise, Q_1 cuts off and class A operation will no longer be maintained.
3. The transfer characteristic of the emitter follower of Fig. 2.9.1 is described by

$$v_o = v_i - v_{BE1}$$

where v_{BE1} depends on the emitter current i_{E1} and thus on the load current i_L .

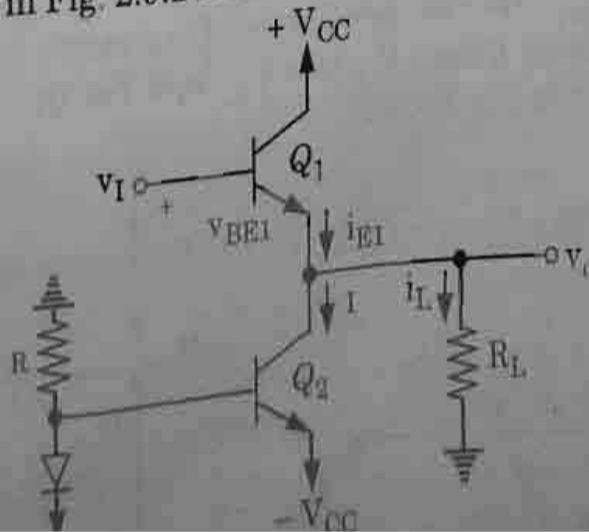4. If we neglect the relatively small changes in v_{BE1} , the linear transfer curve shown in Fig. 2.9.2 results.



5. As indicated, the positive limit of the linear region is determined by saturation of Q_1 , thus

$$v_{o \max} = V_{CC} - V_{CE1sat}$$

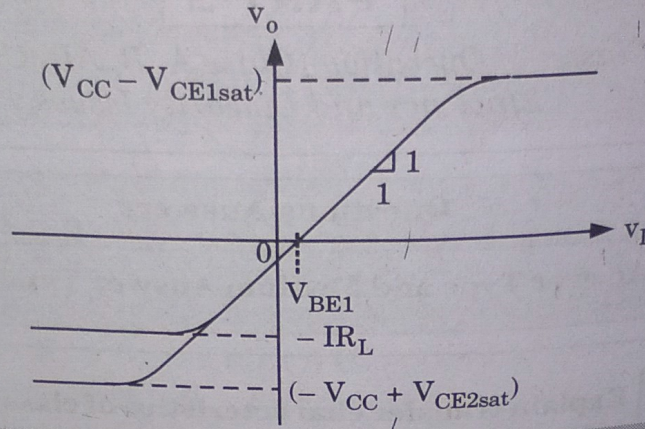


Fig. 2.9.2. Transfer characteristic of the emitter follower.

6. In the negative direction, depending on the values of I and R_L , the limit of the linear region is determined either by Q_1 turning off,

$$v_{o \min} = -IR_L$$

or by Q_2 saturating,

$$v_{o \min} = -V_{CC} + V_{CE2sat} \quad \dots(2.9.1)$$

7. The absolutely lowest output voltage is that given by eq. (2.9.1) and is achieved provided the bias current I is greater than the magnitude of the corresponding load current,

$$I \geq \frac{|-V_{CC} + V_{CE2sat}|}{R_L}$$

Signal waveform

Linearity issues of class AB:-

1. A bias voltage V_{BB} is applied between the bases of Q_N and Q_P . For $v_I = 0$, $v_o = 0$, and a voltage $V_{BB}/2$ appears across the base-emitter junction of each of Q_N and Q_P .

2. Assuming matched devices,

$$i_N = i_P = I_Q = I_S e^{V_{BE}/2V_T} \quad \dots(2.13.1)$$

3. When v_I goes positive by a certain amount, the voltage at the base of Q_N increases by the same amount and the output becomes positive at an almost equal value,

$$v_o = v_I + \frac{V_{BB}}{2} - v_{BE_N} \quad \dots(2.13.2)$$

4. The positive v_o causes a current i_L to flow through R_L , and thus i_N must increase i.e.,

$$i_N = i_P + i_L$$

The increase in i_N will be accompanied by a corresponding increase in v_{BE_N} .

$$\dots(2.13.3)$$

5. Since the voltage between the two bases remains constant at V_{BB} , the increase in v_{BE_N} will result in an equal decrease in v_{BE_P} and hence in i_P . The relationship between i_N and i_P can be derived as follows.

$$v_{BE_N} + v_{BE_P} = V_{BB}$$

$$V_T \ln \frac{i_{Q_n}}{I_Q} + V_T \ln \frac{i_{Q_p}}{I_Q} = 2V_T \ln \frac{I_Q}{I_Q}$$

$$i_{Q_n} i_{Q_p} = I_Q^2 \quad \dots(2.13.4)$$

6. Eq. (2.13.3) and (2.13.4) can be combined and we get

$$i_{Q_n}^2 - i_{L} i_{Q_n} - I_Q^2 = 0 \quad \dots(2.13.5)$$

7. For positive output voltages, the load current is supplied by Q_p , which acts as the output emitter follower. Meanwhile, Q_n will be conducting a current that decreases as v_o increases, for large v_o the current in Q_n can be ignored altogether.
8. For negative input voltages the opposite occurs, the load current will be supplied by Q_n which acts as the output emitter follower, while Q_p conducts a current that gets smaller as v_i becomes more negative. Eq. (2.13.4), relating i_{Q_n} and i_{Q_p} holds for negative inputs as well.
9. We conclude that the class AB stage operates in much the same manner as the class B circuit, with one important exception. For small v_i , both transistors, and as v_i is increased or decreased, one of the two transistors takes over the operation.
10. Since the transition is a smooth one, crossover distortion will be almost totally eliminated. Fig. 2.13.1 shows the transfer characteristic of the class AB stage.

