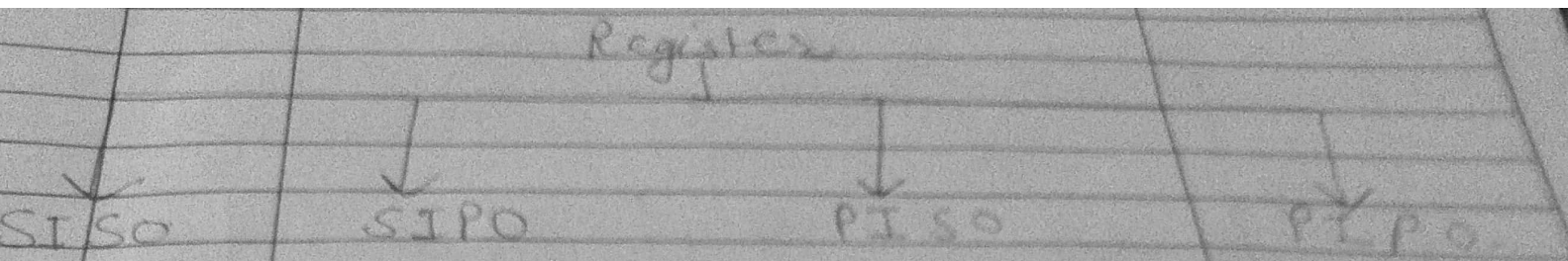


class B Tech 3rd yrs (ECL)
Subt ADV
Faculty Pandeep Singh
Date: 8/1/2020

Topic : Register

Register :- To increase the storage capacity in terms of number of bit we have used a group of flip flop. Such a group of flip flops is known as a register.

* Thus register is a group of flip flops. The "n-bit" register will consists of "n" number of flip flop and it is capable of storing an "n-bit" word.




Buffer Register:

The simplest type of register constructed using four D-flip flops is shown in fig. This is a 4-bit register, but we can construct an n -bit register by following the same principle. This register is also called as the buffer register.

* In other words the Buffer Register are used for temporary.

Class Subject

Storage of digital words

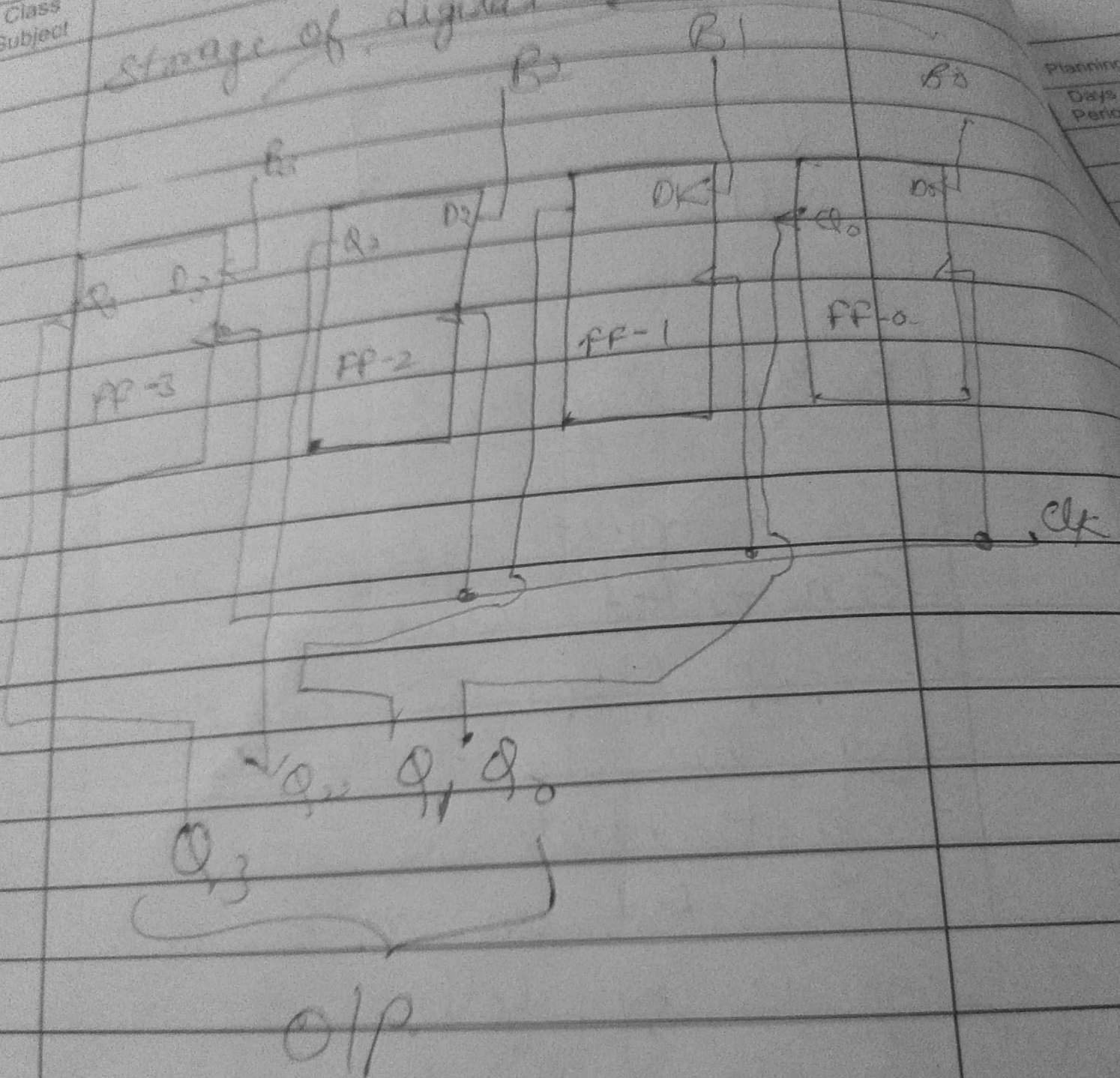

VHDL Code for SIPO

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity Sipo is
```

```
port (clk, clear : in std_logic;
```

```
input_data : in std_logic;
```

```
Q : out std_logic_vector (3 downto 0));
```

```
end Sipo;
```

Architecture behaviour of Sipo is

```
begin
```

```
process (clk).
```

```
begin
```

```
if clear = '1' then
```

```
Q <= "0000";
```

elsif (clk'event and clk = '1')

Q(3 downto 0) <= Q(2 downto 0);

Q(0) <= Input_Data;

end if;

end process;

end behaviour;