


Unit IV [Digital to analog converters]

A DAC converts an abstract finite-precision number (usually a fixed point binary number) into a physical quantity (e.g. a voltage or a pressure etc) in particular.

DACs are often used to convert finite-precision time series data to a continuous varying physical signal.

An ideal DAC converts the abstract numbers into a conceptual sequence of impulse that are then processed by a reconstruction filter (it is used to construct a smooth analog signal from a digital input)

functional diagram of 8-bit DAC.

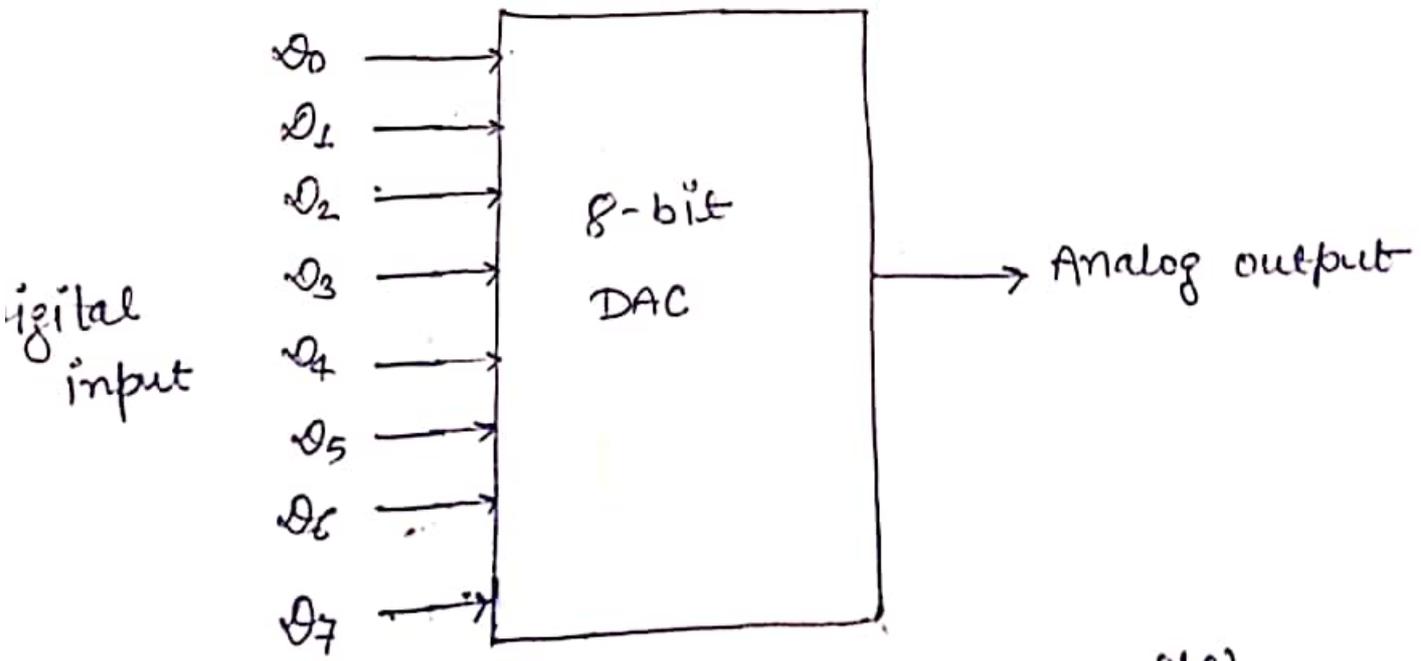

sample with process - $f(t)$ (input)



Converted in impulse discrete signal.



A digital to analog converter converts digital input signal into an analog output signal. The digital signal is represented with a binary code which is 0 and 1. In general, the number of binary input will be a power of two.

Common Types of DACs


① Binary Weighted resistor DAC

② R-2R Ladder DAC
Other types of DACs

③ * Pulse width modulator

④ * Oversampling DACs or interpolating DACs

* Binary weighted DACs

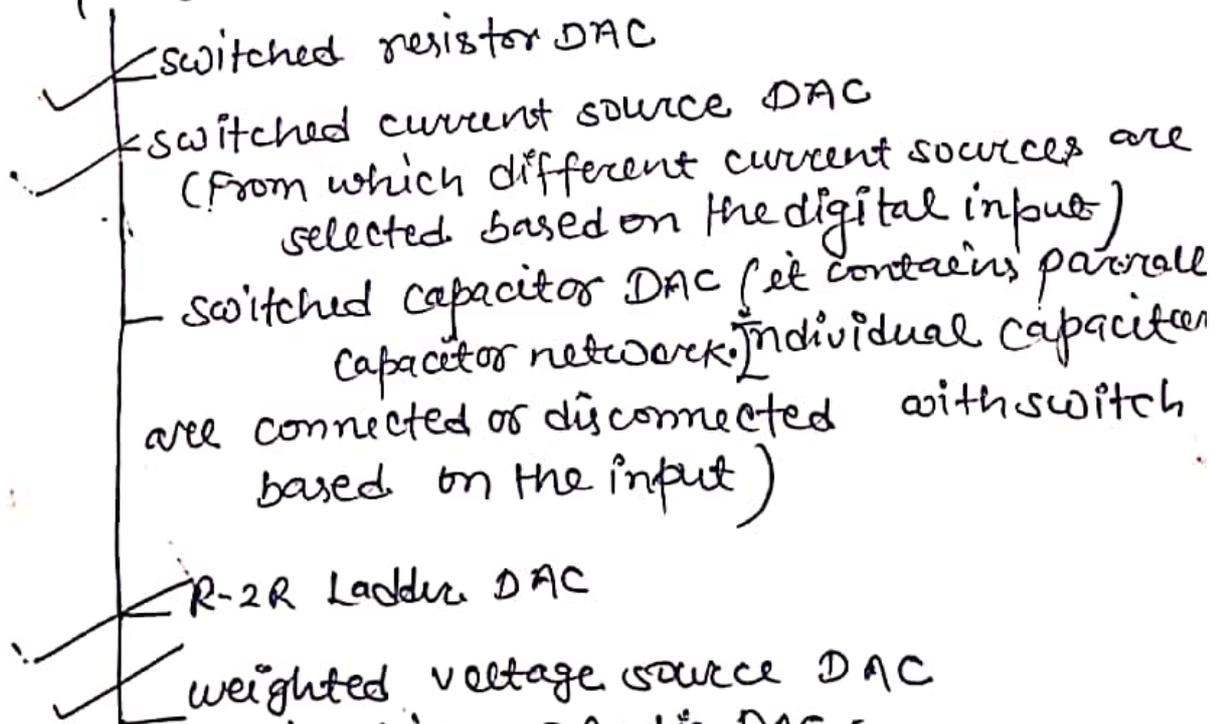

⑤ Successive approximation or cyclic DAC

⑥ Thermocoded DAC

⑦ Hybrid DACs - - - - many