


# UNIT-4 >>CURRENT MIRROR AND OP-AMP DESIGN

## SUBJECT-ANALOG CIRCUIT

### LECTURE-1>>CURRENT MIRROR
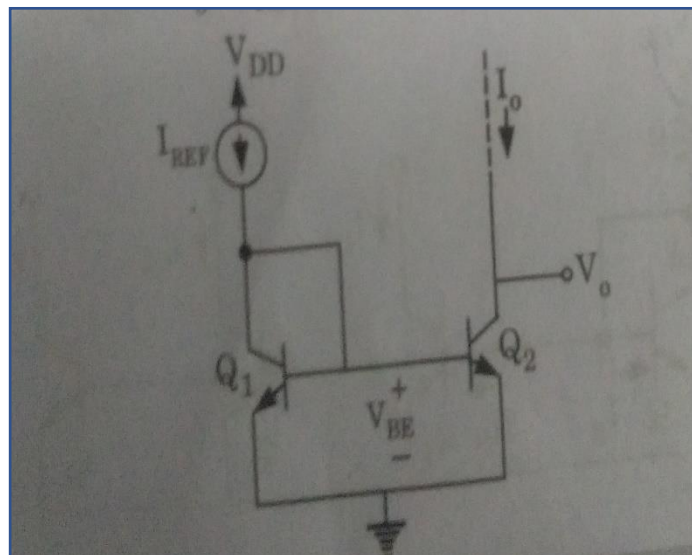
#### BJT CURRENT MIRROR

The basic BJT current mirror is shown in fig



Consider  $\beta$  is high and neglect base current  $I_{REF}$  is passed through  $Q_1$  and the corresponding voltage is  $V_{BE}$ .  $V_{BE}$  is applied voltage between base and emitter of  $Q_2$ .

Now,  $Q_2$  is matched to  $Q_1$ , i.e. same relative area of emitter-base junction and having equal collector current.

Here,  $Q_2$  is in active mode until  $V_o$  is 0.3v or higher than emitter voltage.

For obtaining the current transfer ratio, it is required to consider  $m$  times relative area of emitter-base junction (EBJ).

$$I_o = m I_{REF}$$

The current transfer ratio,

$$I_o \div I_{REF} = I_{s2} \div I_{s1} = \text{Area of EBJ of } Q_2 \div \text{Area of EBJ of } Q_1$$

From the node equation at collector of  $Q_1$ ,

$$I_{REF} = I_C = 2I_C / \beta$$


Since  $I_o = I_C$

$$I_o \div I_{REF} = I_C / I_C (1 + 2I_C / \beta)$$
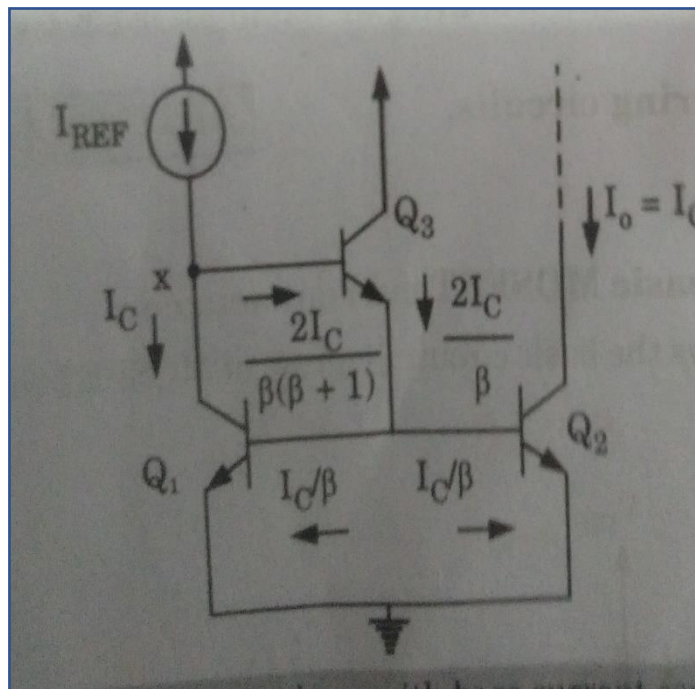
### BASE CURRENT MIRROR

A bipolar current mirror with a current transfer ratio is less dependent on  $\beta$  than that of simple current mirror.

This reduces dependency on  $\beta$  and is achieved by using transistor  $Q_3$ . The  $Q_3$  supplies the base current to the  $Q_1$  and  $Q_2$ .



The sum of base currents divided by ( $\beta_3$ ) resulting in much smaller error current, that has to be supplied by  $I_{REF}$ .

Let us assume Q and Q are matched and having equal collector current.

A node equation at node x gives

$$I_{REF} = I_C [1 + 2/\beta(\beta + 1)]$$

As,  $I_o = I_C$

The current transfer ratio of the mirror will be

$$I_o/I_{REF} = 2/1 + \beta(\beta + 1) = 1/1 + 2/\beta^2 \quad \text{eq.3}$$

Eq.3 shows that the error due to finite  $\beta$  has been reduced from  $2/\beta$  to  $2/\beta^2$

However, the output resistance ( $R_o$ ) remains approximately equal to that of simple mirror.

IF  $I_{REF}$  is not present, then we connect node x to the power supply  $V_{CC}$  through resistor R, then

$$I_{REF} = \frac{V_{CC} - V_{BE1} - V_{BE3}}{R}$$

### **CHARACTERISTICS OF CURRENT MIRROR: -**

- More accurate current transfer ratio.
- Highly output resistance.