

①


## Unit IV [Digital to analog converters]

A DAC converts an abstract finite-precision number (usually a fixed point binary number) into a physical quantity (e.g. a voltage or a pressure etc) in particular.


DACs are often used to convert finite-precision time series data to a continuous varying physical signal.

An ideal DAC converts the abstract numbers into a conceptual concept sequence of impulse that are then processed by a reconstruction filter (it is used to construct a smooth analog signal from a digital input)

functional diagram of 8-bit DAC.

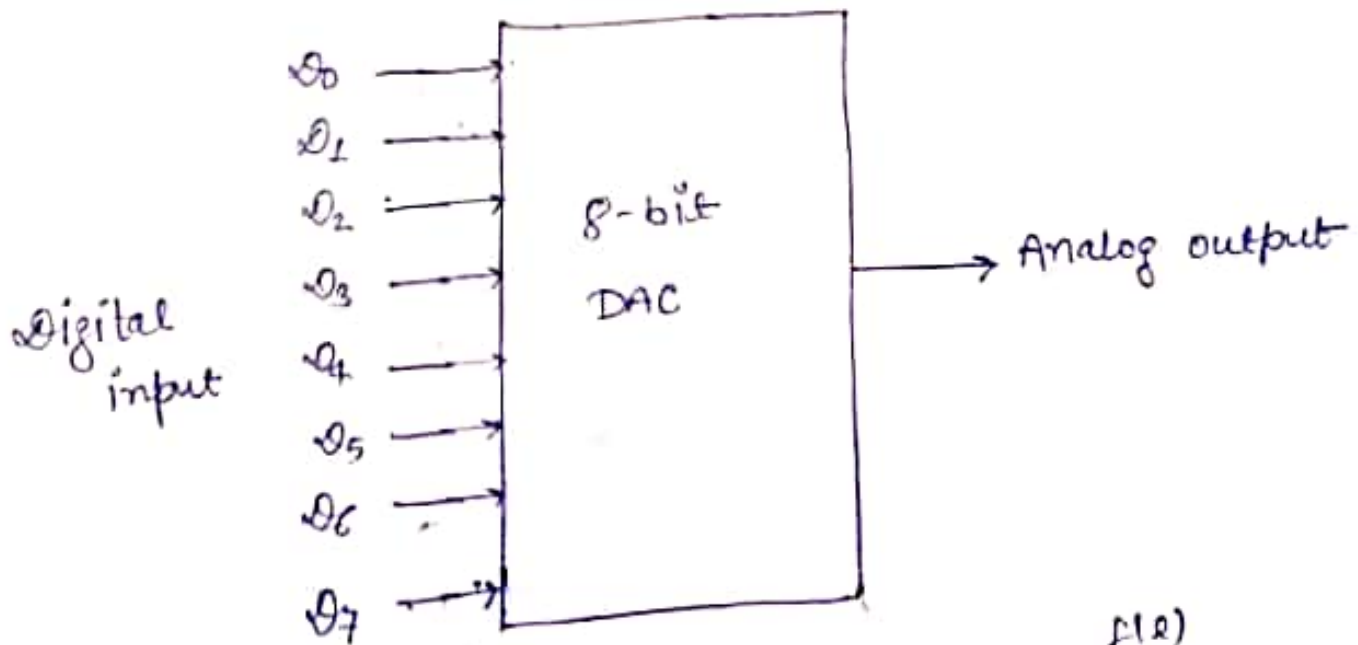

Example with process -

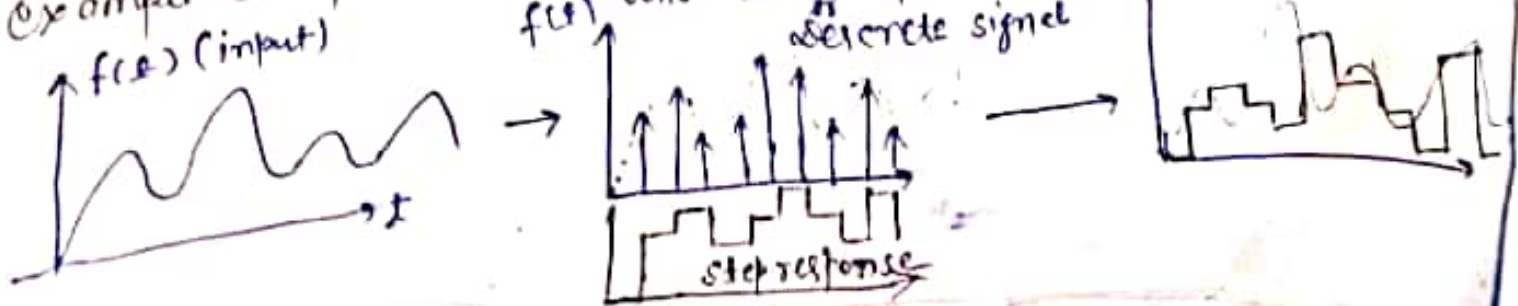


A digital to analog converter converts digital input signal into an analog output signal.

The digital signal is represented with a binary code which is 0 and 1 in general, the number of binary input will be a power of two.

Common Types of DACs

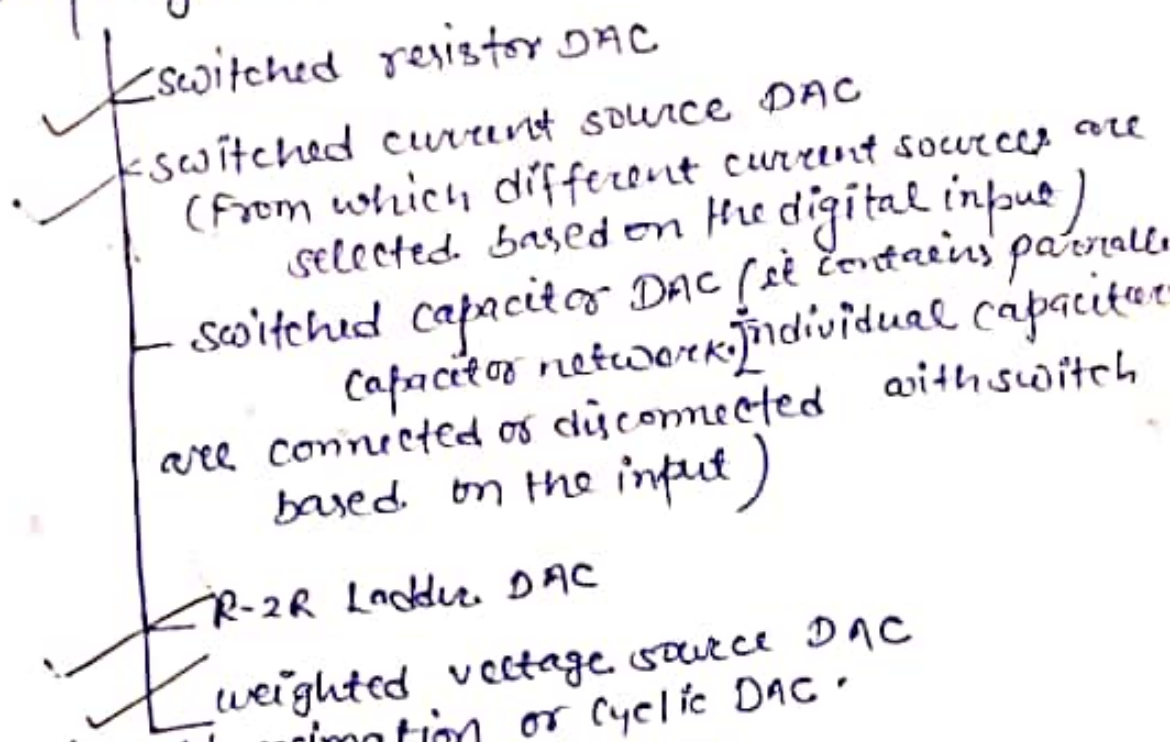- ① Binary Weighted resistor DAC
- ② R-2R Ladder DAC
- ③ other types of DACs
- ④ \* Pulse width modulator
- ⑤ \* oversampling DACs or interpolating DACs
- \* Binary weighted DACs



- ⑥ Successive approximation or cyclic DAC
- ⑦ Thermocoded DAC
- ⑧ Hybrid DACs ----- many