

Ques=1 Define Transconductance.

Ques=2 Define benefits of h-Parameters.

Ques=3 Briefly explain why dominant pole high frequency Compensation method Used in amplifier.

Ques=4 Define Current gain.

Ques=5 Write the equations for the Output voltage and Voltage gain for CD Amplifier.

Ques=6 Why thermal Runaway is not there in mosfet.

Ques=7 Draw the low frequency Simplified h-Parameters model of an amplifier with a V_{in} bypassed emitter resistor.

Ques=8 Give the voltage gain for CE Configuration Including source resistance.



Assignment 2

- Ques=1 What are the techniques used to improve input impedance.
- Ques=2 Define voltage gain.
- Ques=3 Give the voltage gain for CE configuration including source resistance.
- Ques=4 Why N-channel FET's have a better response than P-channel FET's.
- Ques=5 Write the equation for the output voltage and voltage gain for CB amplifier.
- Ques=6 Briefly explain why dominant pole high frequency compensation method is used in amplifier.
- Ques=7 Give two advantages of common source FET amplifier.
- Ques=8 Why an NPN transistor has a better high frequency response than the PNP transistor.

